


Assignment 2

CSE 251


Name: Mazidul Islam Kabbo

ID: 24301500

7b)

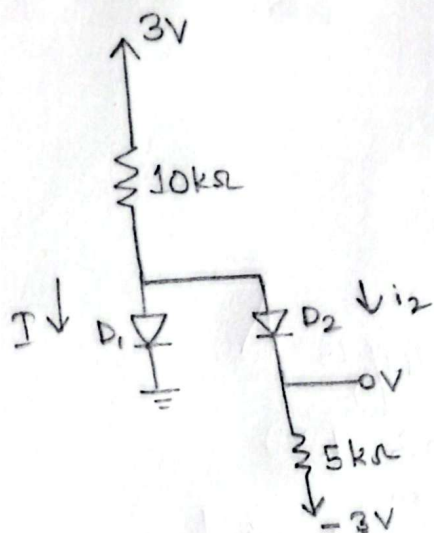

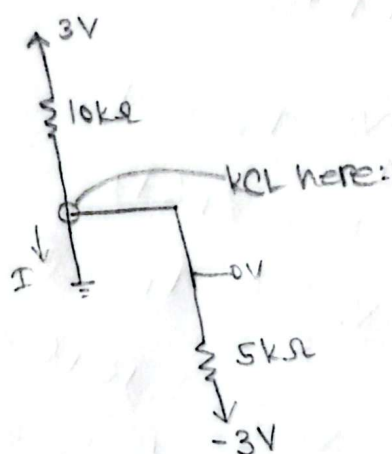lets assume, $D_1 = \text{on}$, $D_2 = \text{on}$




$$V = 0V$$

$$\frac{3-0}{10} = I + \frac{0-(-3)}{5}$$

$\frac{3}{10} - \frac{3}{5} = I = -\frac{3}{10}$, since current is negative, D_1 cannot be on,

$$i_2 = \frac{0-(-3)}{5} = \frac{3}{5}, D_2 \text{ may be on}$$

lets assume D_1 is off and D_2 is on

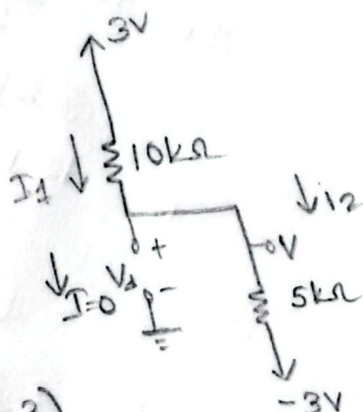

$$\frac{3-V}{10} = \frac{V-(-3)}{5}$$

$$\frac{3-V}{10} = \frac{V+3}{5}$$

$$\frac{3-V}{2} = V+3$$

$$3-V = 2V+6$$

$$-3 = 3V$$

$$V = -1$$

$$i_2 = \frac{-1-(-3)}{5}$$


$= \frac{2}{5}$, so D_2 may be on

$$V_d = -1 - 0$$

$= -1$, so D_1 may be off.


since both assumptions correct, $D_1 = \text{off}$, $D_2 = \text{on}$,

$$I = 0, V = -1V$$

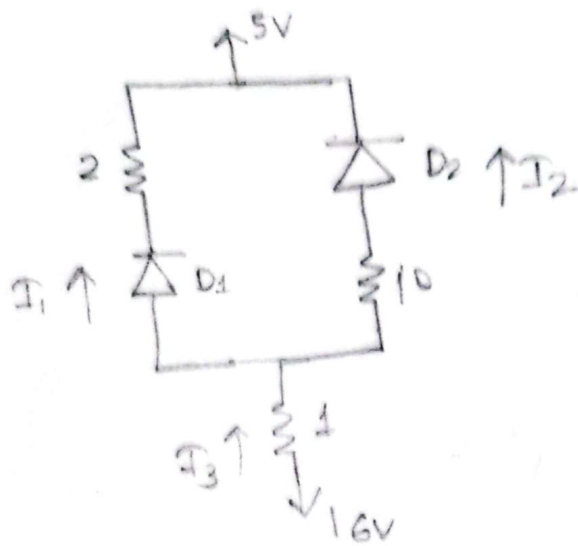

$$V_{D0} = 0.7V$$

lets assume, D_1 and D_2 on.

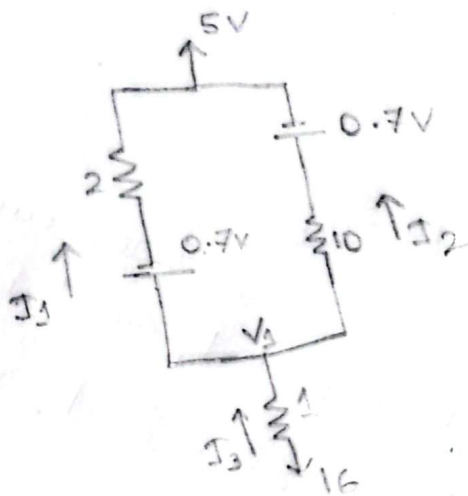

$$I_3 = I_2 + I_1$$

$$\frac{16 - V_1}{1} = I_3 \quad \text{--- (I)}$$

$$V_1 - 5 = 0.7 + 2I_1$$

$$\frac{V_1 - 5.7}{2} = I_1 \quad \text{--- (II)}$$

$$V_1 - 5 = I_2 \cdot 10 + 0.7$$

$$\frac{V_1 - 5.7}{10} = I_2 \quad \text{--- (III)}$$

$$I_1 = \frac{12.1375 - 5.7}{2}$$

$$= 3.21875 \text{ mA}$$

$$I_2 = \frac{12.1375 - 5.7}{10}$$

$$= 0.64375 \text{ mA}$$

$$I_3 = 3.8625 \text{ mA}$$

$$16 - V_1 = \frac{V_1 - 5.7}{10} + \frac{V_1 - 5.7}{2}$$

$$16 - V_1 = \frac{V_1 - 5.7 + 5V_1 - 28.5}{10}$$

$$160 - 10V_1 = 6V_1 - 34.2$$

$$194.2 = 16V_1$$

$$V_1 = 12.1375$$


Since both I_1 and $I_2 > 0$, assumptions are correct.

$$I_1 = 3.22 \text{ mA}$$


$$I_2 = 0.64 \text{ mA}$$

$$I_3 = 3.86 \text{ mA}$$

16.

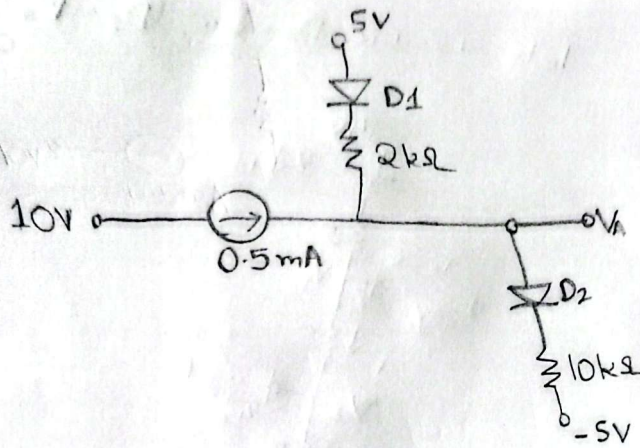

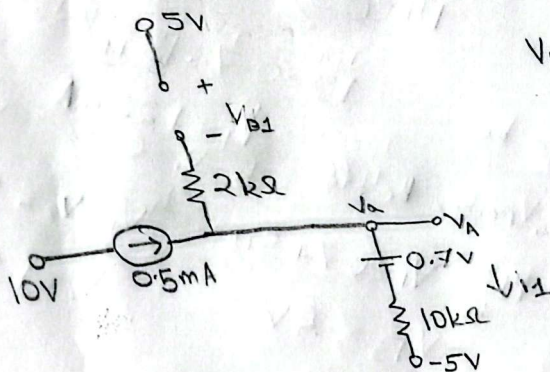lets assume, $D_1 = \text{off}$, $D_2 = \text{on}$



$$V_{D1} = 0.7V$$

$$V_a + 5 = 0.7 + I \cdot 10$$

$$\frac{V_a + 4.3}{10} = I$$

✓ KCL at V_a

$$0.5 + 0 = \frac{V_a + 4.3}{10}$$

$$5 = V_a + 4.3$$


$$V_a = 0.7$$

$$i_1 = \frac{0.7 + 4.3}{10} = 0.5, \text{ so}$$

D_2 may be on

$V_{D1} = 5 - 0.7$
 $= 4.3V$, this is greater than
 $0.7V$, so this assumption
 is wrong.

Assuming
 $D_1, D_2 = \text{on}$

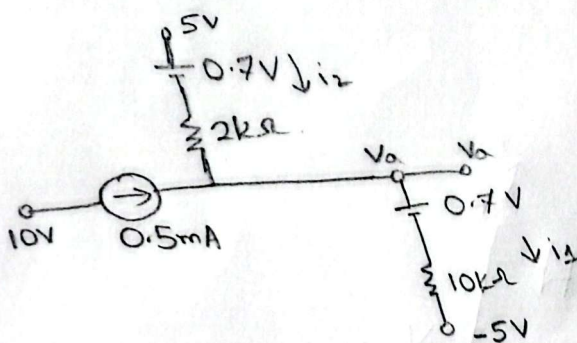

$$0.5 + i_2 = i_1$$

$$\begin{cases} 5 - V_a = 0.7 + i_2 \times 2 \\ \frac{4.3 - V_a}{2} = i_2 \end{cases}$$

$$0.5 + \frac{4.3 - V_a}{2} = \frac{V_a + 4.3}{10}$$

$$0.5 = \frac{V_a + 4.3}{10} + \frac{V_a - 4.3}{2}$$

$$0.5 = \frac{V_a + 4.3 + 5V_a - 21.5}{10}$$

$$5 = 6V_a - 17.2$$

$$6V_a = 22.2$$


$$V_a = 3.7V$$

$$i_2 = 0.3mA$$


$$i_1 = 0.8mA$$

$\therefore$ both assumptions correct
 and $V_a = 3.7V$, $D_1, D_2 = \text{on}$

18.

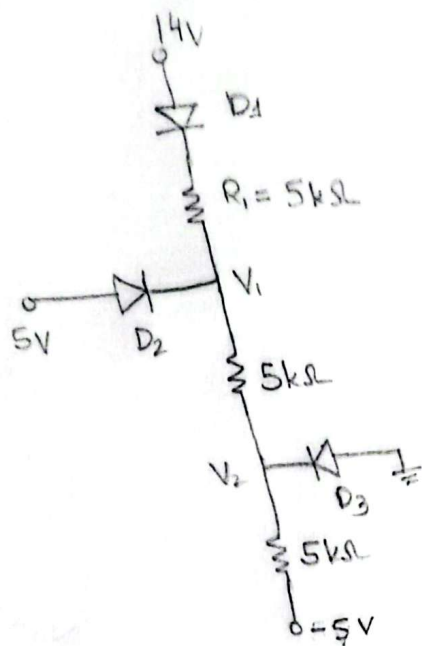

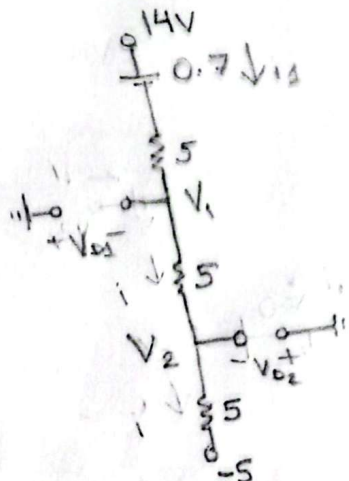lets assume, $D_1 = \text{on}$, $D_2 = D_3 = \text{off}$



$$14 - (-5) = 0.7 + 5i_1 + 5i_1 + 5i_1$$

$$19 - 0.7 = 15i_1$$

$$i_1 = 1.22 \text{ mA}$$

$i_1 > 0$, so D_1 may be on,

$0 - V_1 = -7.2 < 0.7$, so D_2 may be off

$0 - V_2 = -1.1 \text{ V} < 0.7$, so

D_3 may be off.

$$14 - V_1 = 0.7 + 5i_1$$

$$V_1 = 7.2 \text{ V}$$

$$V_1 - V_2 = 5i_1$$


$$V_2 = 1.1$$

$$V_1 - V_2 = 6.1 \text{ V}$$


Since all assumption correct

$D_1 = \text{on}$, $D_2 = D_3 = \text{off}$, $V_2 = 6.1 \text{ V}$ (Ans)

1iii) $(A+C) \cdot (B+D)$

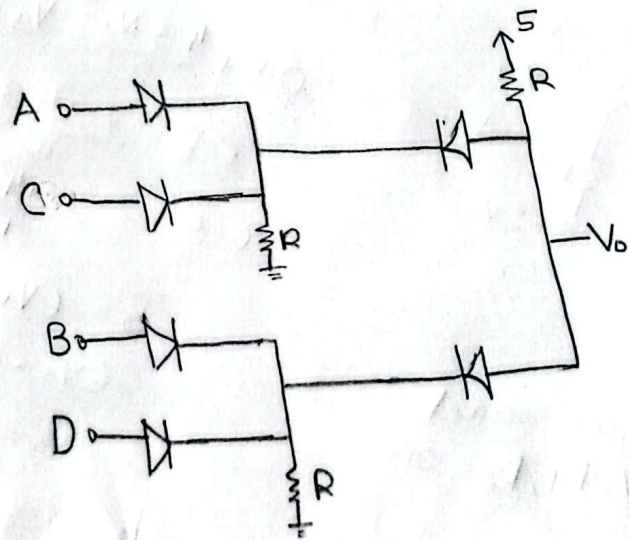

10.

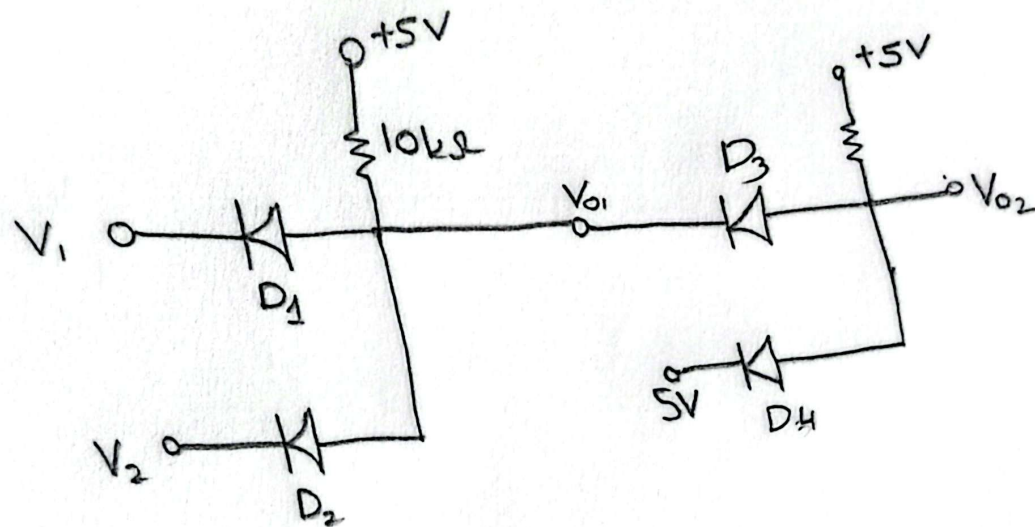

$$V_1 = 3V$$

$$V_2 = 1V$$

$$V_0 = 0.7V$$

$$V_{01} = \min(3 + 0.7, 1 + 0.7)$$

$$= 1.7$$

$$V_{02} = \min(5 + 0.7, 1.7 + 0.7)$$

$$= 2.4V$$

$$V_{02} = (V_1 \cdot V_2) \times 1$$

$$= V_1 \cdot V_2$$