

Student ID:	24301500	Lab Section:	7B
Name:	Majidul Islam Kabbo	Lab Group:	6

Experiment-02

Study of Op-Amp: Introduction to Op-Amp, Comparator Circuits, Non-Inverting Amplifier, Inverting Amplifier, Inverting Summing Amplifier & their VTCs



Inspiring Excellence

CSE251 - Electronic Devices and Circuits Lab

Objective


1. To understand the basic principles and characteristics of an Operational Amplifier (Op-Amp)
2. To understand Operational Amplifier (Op-Amp) as a Comparator and investigate its use
3. To investigate the use of Operational Amplifier (Op-Amp) as Non-Inverting Amplifier, Inverting Amplifier and Inverting Summing Amplifier

Equipment

1. Op-Amp ($\mu A741$)
2. Resistance ($1k\Omega$, $2.7k\Omega$, $10k\Omega$)
3. DC Power Supply
4. Function Generator
5. Digital Multimeter
6. Trainer Board, Breadboard, Chords and Wires

Background Theory

Introduction

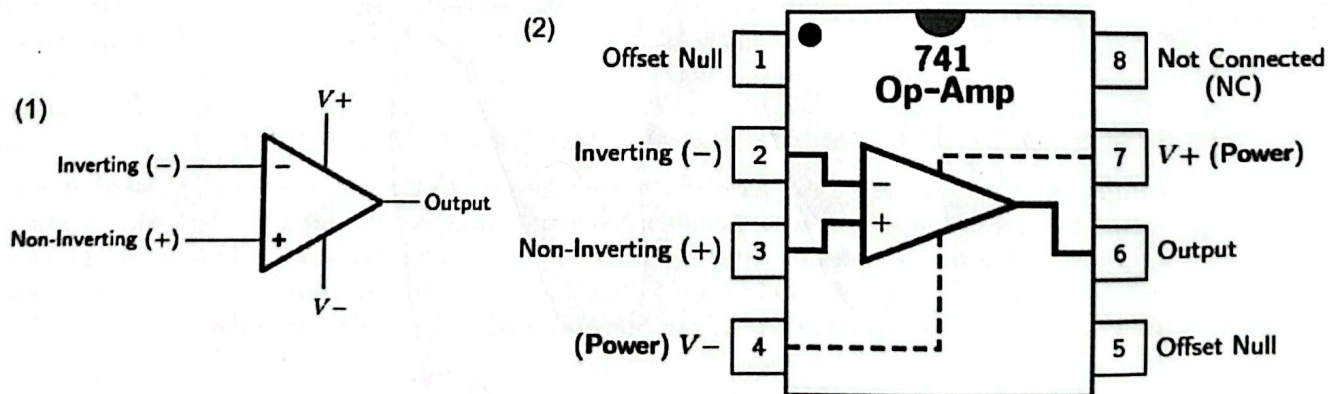

(1) Op-Amp Simplified Circuit Symbol (2) Op-Amp IC Pin Diagram

One of the most widely used electronic devices in linear applications is the Operational Amplifier, commonly known as the Op-Amp. An Op-Amp is an integrated circuit that amplifies the difference between two input voltages and produces a single output. We can also do various mathematical operations like addition, subtraction, multiplication, integration, differentiation etc. with the help of Op-Amp. With the addition of suitable external components, Op-Amp can be used for a variety of applications. The figure above shows the simplified circuit symbol of an Op-Amp. There are 2 terminals for input, 1 terminal for output and 2 terminals for power supply.

Task-05: Report

1. Attach the signed Data Sheet (if any)
2. Attach the captured images (if any)
3. Answer the questions in the "Test Your Understanding" section
4. Add a brief Discussion regarding the experiment. For the Discussion part of the lab report, you should include the answers of the following questions in your own words:

- What did you learn from this experiment? — *How to connect and use opamp in three ~~two~~ easy ways*
- What challenges did you face and how did you overcome the challenges? (if any)
- What mistakes did you make and how did you correct the mistakes? (if any) — *wrong connections, changed connection to fix it*
- How will this experiment help you in future experiments of this course?
helped me get a foundational idea on an operational circuit element.

Data Sheet

For Task-02:

Quantity	Value
Value of R_1 using multimeter	0.981
Value of R_2 using multimeter	2.65
Input Amplitude from Oscilloscope, $v_I = \frac{Pk-Pk}{2}$ (use the Measure button of the Oscilloscope)	2.08 1.04
Output Amplitude, $v_O = \frac{Pk-Pk}{2}$ (use the Measure button of the Oscilloscope)	7.92 3.92
Output Amplitude, $v_O = (1 + \frac{R_2}{R_1}) \times v_I$ (theoretical calculation)	3.7

For Task-03:

Quantity	Value
Value of R_1 using multimeter	981
Value of R_2 using multimeter	2.65
Input Amplitude from Oscilloscope, $v_I = \frac{Pk-Pk}{2}$ (use the Measure button of the Oscilloscope)	1
Output Amplitude, $v_O = \frac{Pk-Pk}{2}$ (use the Measure button of the Oscilloscope)	2.76
Output Amplitude, $v_O = -(\frac{R_2}{R_1}) \times v_I$ (theoretical calculation)	-2.7

For Task-04:

Quantity	Value
Value of R_1 using multimeter	9.88
Value of R_2 using multimeter	9.9
Value of R_F using multimeter	9.96
from multimeter, v_{I1}	0.998
from multimeter, v_{I2}	1.971
Output Amplitude from multimeter, v_O	-2.995
Output Amplitude from equation, $v_O = -(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2})$	-2.989

Zeal
22/10/25


Signature of the lab faculty

Test Your Understanding

Answer the following questions:


1. You are given an Op-Amp comparator with $v_1 = 4 \text{ V}$ (p-p) sine wave and $v_2 = V_{REF} = -1 \text{ V}$. Draw the waveform of v_1 , v_2 and v_o in the same graph with proper labels.

Answer:

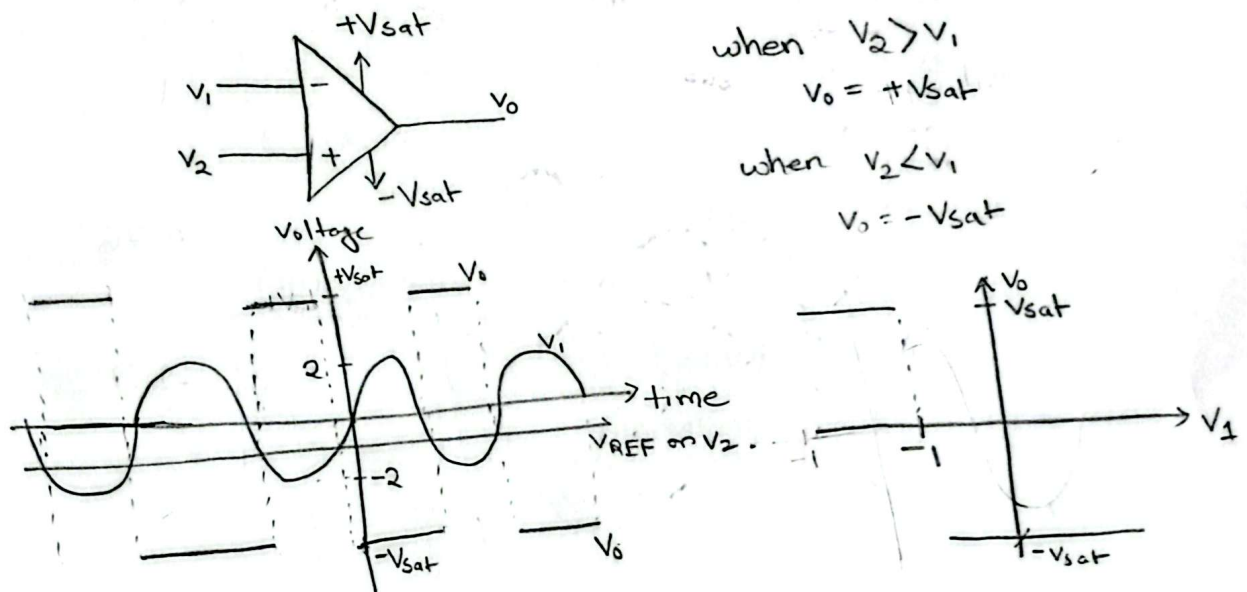


2. You are given an Op-Amp comparator with $v_i = 2 \sin(t)$, where the two ends of the input voltage, v_i (sinusoidal source) is connected to v_1 and v_2 of Op-Amp. Draw the waveform of v_{AC} and v_o in the same graph with proper labels.

Answer:

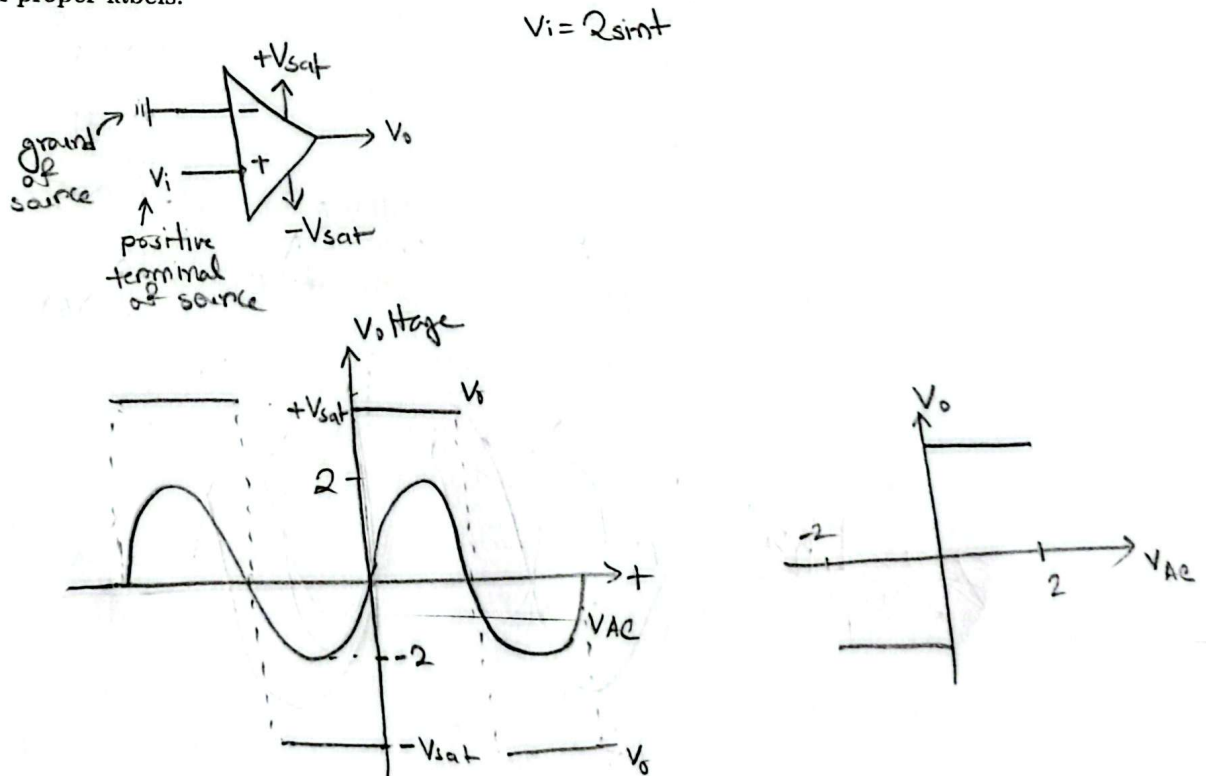


3. You are given an inverting amplifier with $v_i = 4\text{ V}$ (p-p) sine wave, $R_1 = 1\text{ k}\Omega$, $R_2 = 2.2\text{ k}\Omega$. Draw the waveform of v_i and v_o in the same graph with proper labels.

Answer:

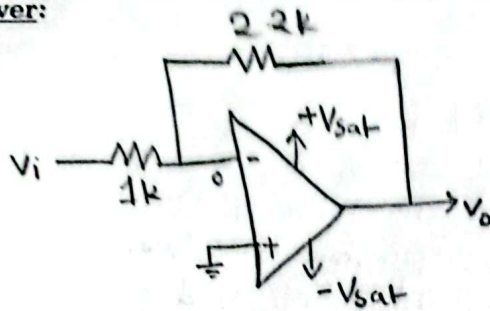

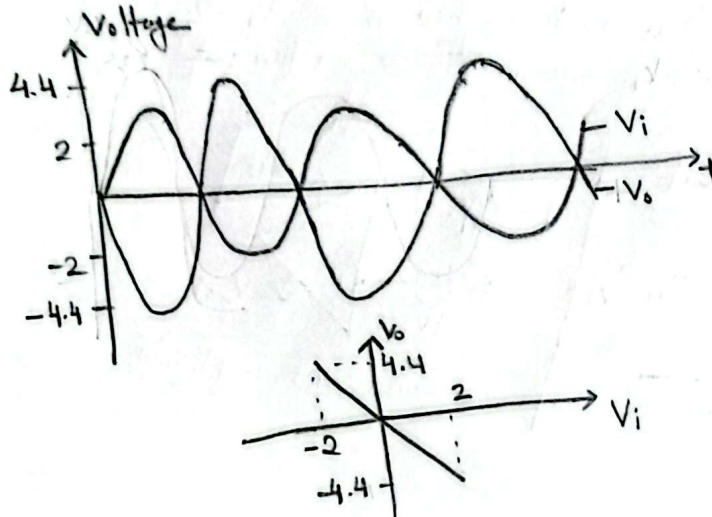
$$V_o = -\frac{R_F}{R_i} \times V_i = -2.2 V_i$$




4. You are given a non-inverting amplifier with $v_i = 4\text{ V}$ (p-p) sine wave, $R_1 = 1\text{ k}\Omega$, $R_2 = 2.2\text{ k}\Omega$. Draw the waveform of v_i and v_o in the same graph with proper labels.

Answer:

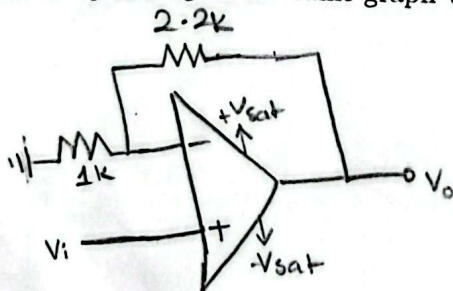

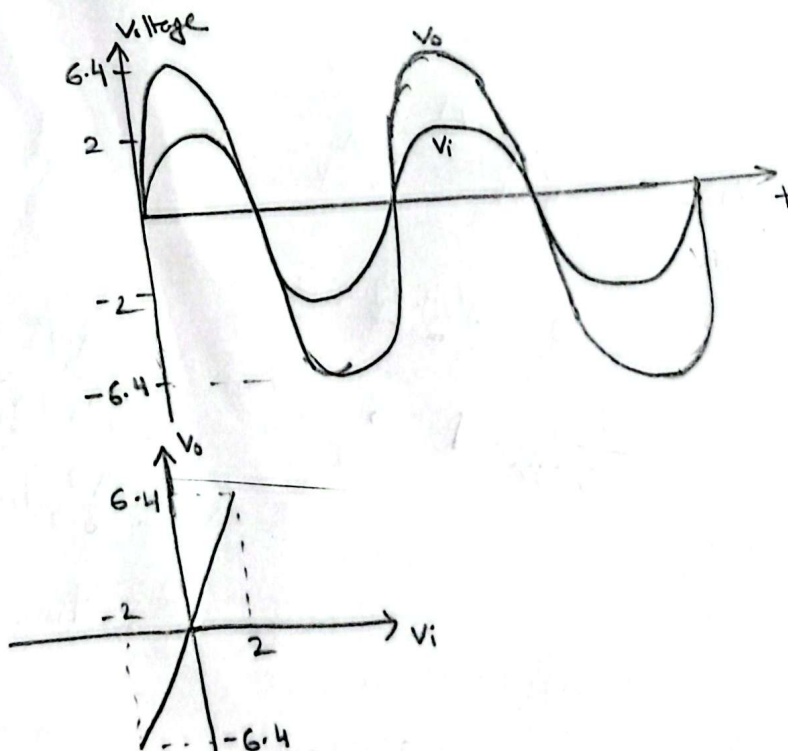
$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_i = 3.2 V_i$$



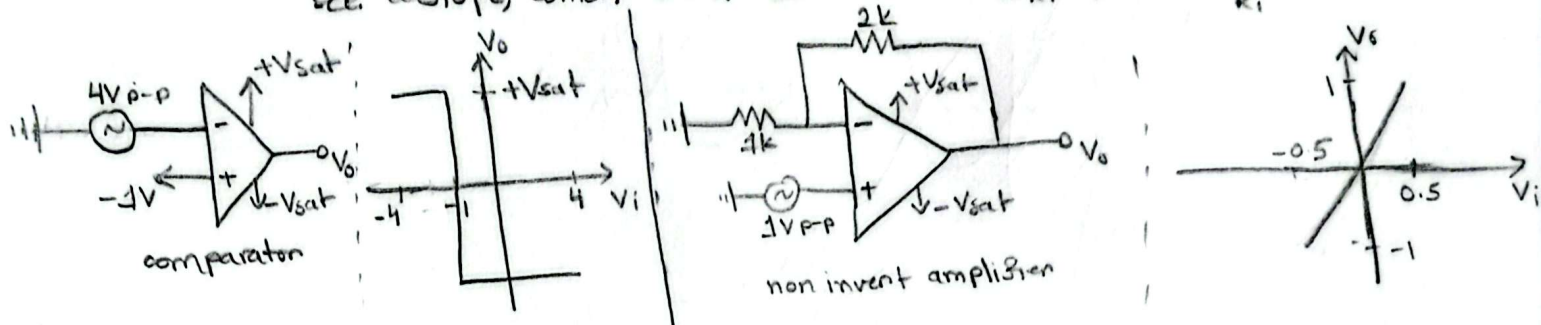
5. Discuss the differences in behavior between the comparator's switching operation and the amplifier's linear scaling. For the comparator, use a 4 V (peak-to-peak) sine wave to the inverting terminal with a fixed reference of -1 V to the non-inverting terminal. For the non-inverting amplifier, set the gain to 2 with a 1 V (peak-to-peak) sine wave input. For each circuit, draw the VTC (i.e., v_{out} vs. v_{in}) on separate graphs with proper labels and discuss accordingly.

Answer: In comparator, the output V_o is $+V_{sat}$ when V_d in input is positive, else its $-V_{sat}$. An OP Amp can amplify a raw V_d to upwards of 10^6 or ∞ in theory, since this value is so high, for very little V_d , this V_o reaches its limit which is $+V_{sat}$ or $-V_{sat}$. So, in comparator V_o almost instantly reaches $+V_{sat}$ or $-V_{sat}$ but in amplifiers, resistors are used to reduce amplification so, the V_d required is much higher to reach $+V_{sat}$, so in VTC we can see a slope, which corresponds to either $(\frac{R_F}{R_i} + 1)$ or $-\frac{R_F}{R_i}$.




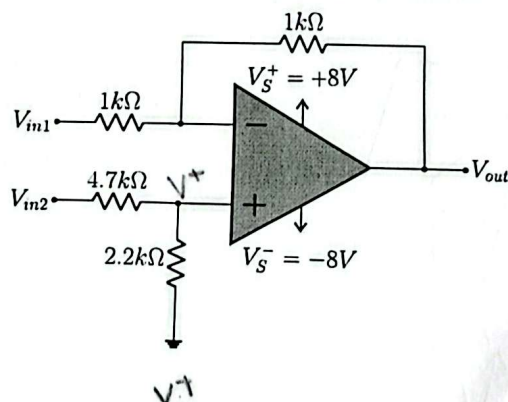6. Deduce the value of V_{out} from the circuit below.

[Hints: Consider the current towards the inverting and non-inverting terminals of Op-Amp is zero, and the voltage of the inverting terminal equals the voltage of the non-inverting terminal]



Answer:

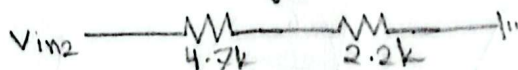

$$V_{in2} - 0 = (I \times 4.7) + 2.2I$$

$$\frac{V_{in2}}{6.9\text{ k}} = I \Rightarrow$$


$$V_{in2} - V^+ = 4.7I$$

$$= \frac{4.7 \times V_{in2}}{6.9}$$

$$V_{in2} - \frac{4.7}{6.9} V_{in2} = V^+$$

$$\frac{2.2}{6.9} V_{in2} = V^+$$

$$V^+ = V^- = \frac{2.2}{6.9} V_{in2}$$

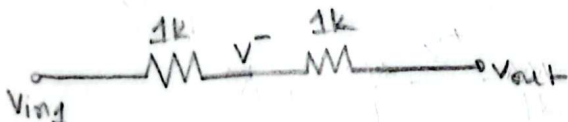

$$\frac{V_{in1} - V^-}{1} = \frac{V^- - V_{out}}{1} \Rightarrow 2V^- - V_{out} = V_{in1}$$

$$2V^- - V_{in1} = V_{out} \Rightarrow V_{out} = \frac{4.4}{6.9} V_{in2} - V_{in1} \text{ [ANS]}$$


GWINSTEK

10k pts

200kSa/s



Trig'd

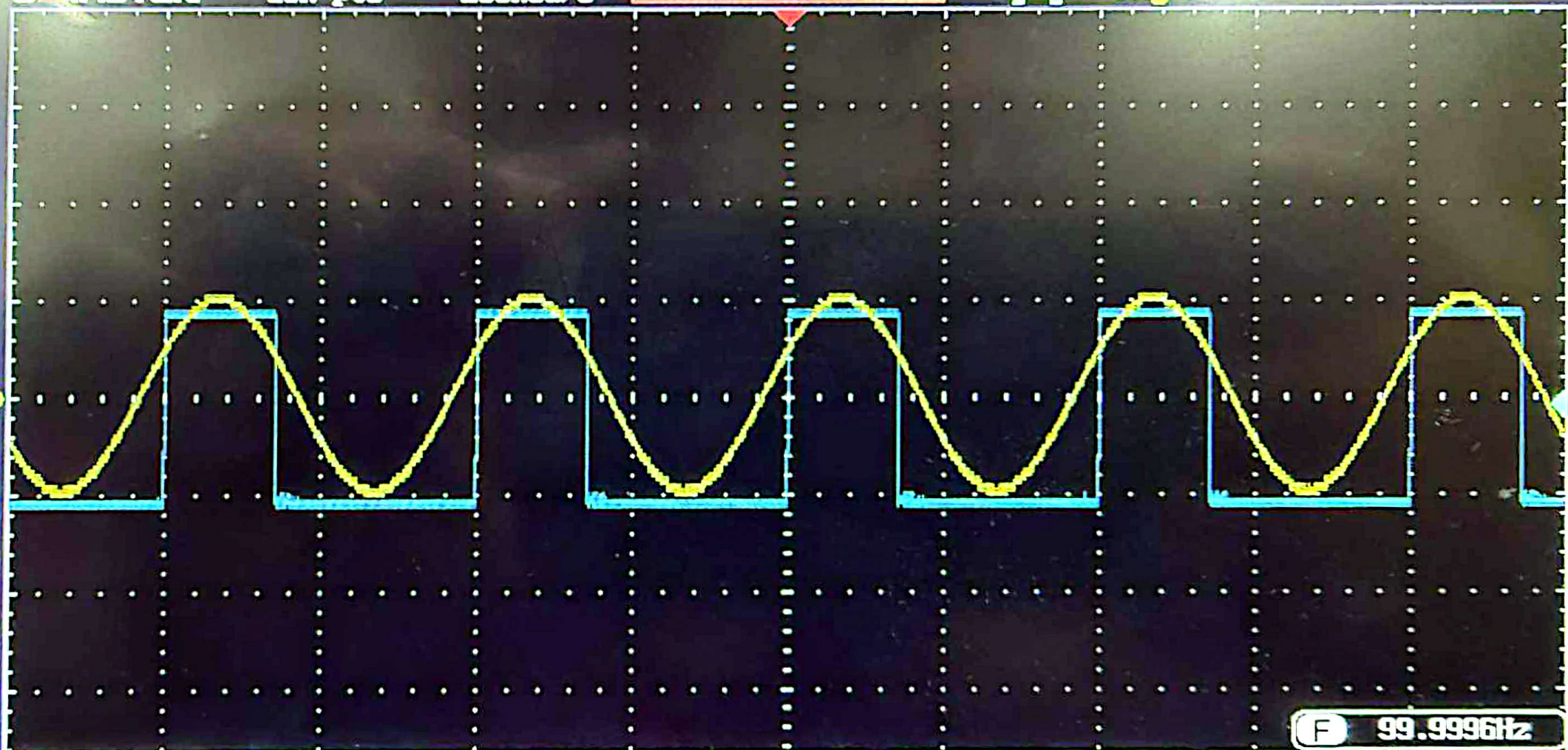

① = 5.00V ② = 10.0V

5ms

0.00000s

② f 99.9996Hz -800mV DC

Mode
Fit Screen
AC Priority

Undo
Autoset

GWINSTEK


10k pts

200kSa/s




Trig'd

1

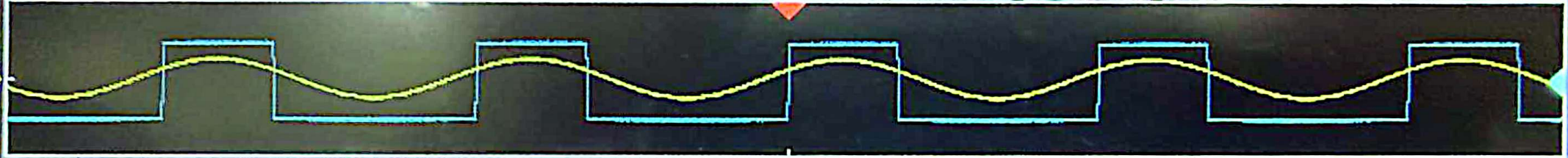

2

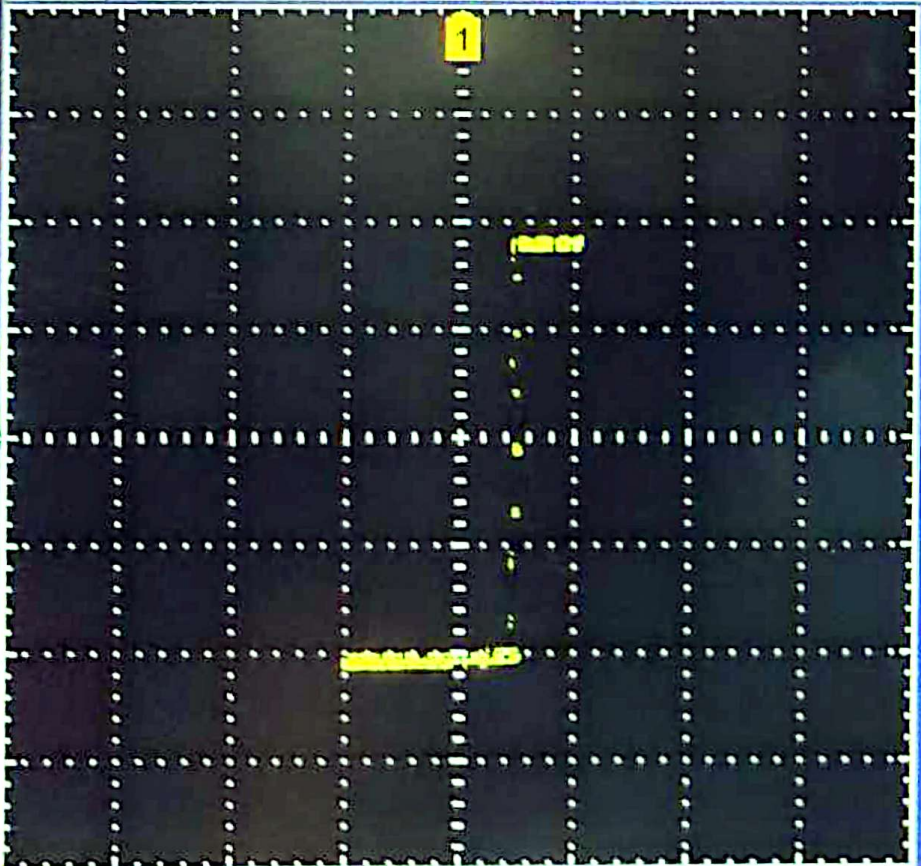

1 = 5.00V 2 = 5.00V

5ns

0.00000s

F 99.9993Hz

2 f -800mV DC

GWINSTEK

10k pts

200kSa/s



Trig'd

Measurement Summary

Pk-Pk	9.80V	Frequency	100.0Hz
Max	5.00V	Period	9.995ms
Min	-4.80V	RiseTime	2.842ms
Amplitude	9.60V	FallTime	3.017ms
High	5.00V	+Width	5.040ms
Low	-4.60V	-Width	4.955ms
Mean	187mV	Dutycycle	50.43%
CycleMean	185mV	+Pulses	5
RMS	3.47V	-Pulses	4
CycleRMS	3.47V	+Edges	5
Area	9.36mVs	-Edges	4
CycleArea	1.86mVs		
ROVShoot	0.00%		
FOVShoot	2.08%		
RPREShoot	2.08%		
FPREShoot	0.00%		

Display All

Source

CH1

OFF

① = 5.00V ② = 5.00V

5ms

0.00000s

②

↑

Add
MeasurementRemove
MeasurementGating
ScreenDisplay All
CH1High-Low
Auto

Statistics

Reference
Levels

GWINSTEK


10k pts

200kSa/s




Trig'd

1

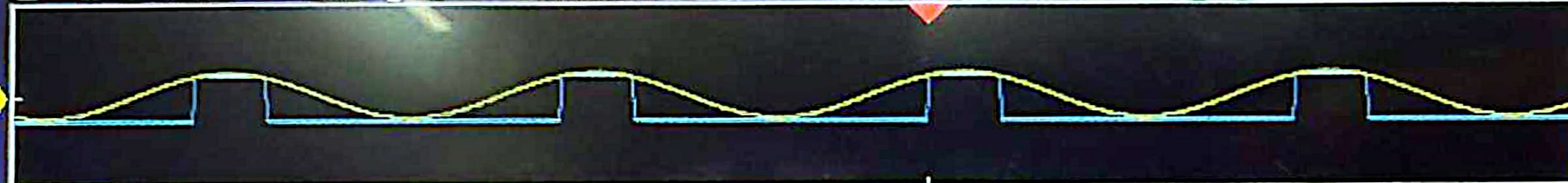

1

2

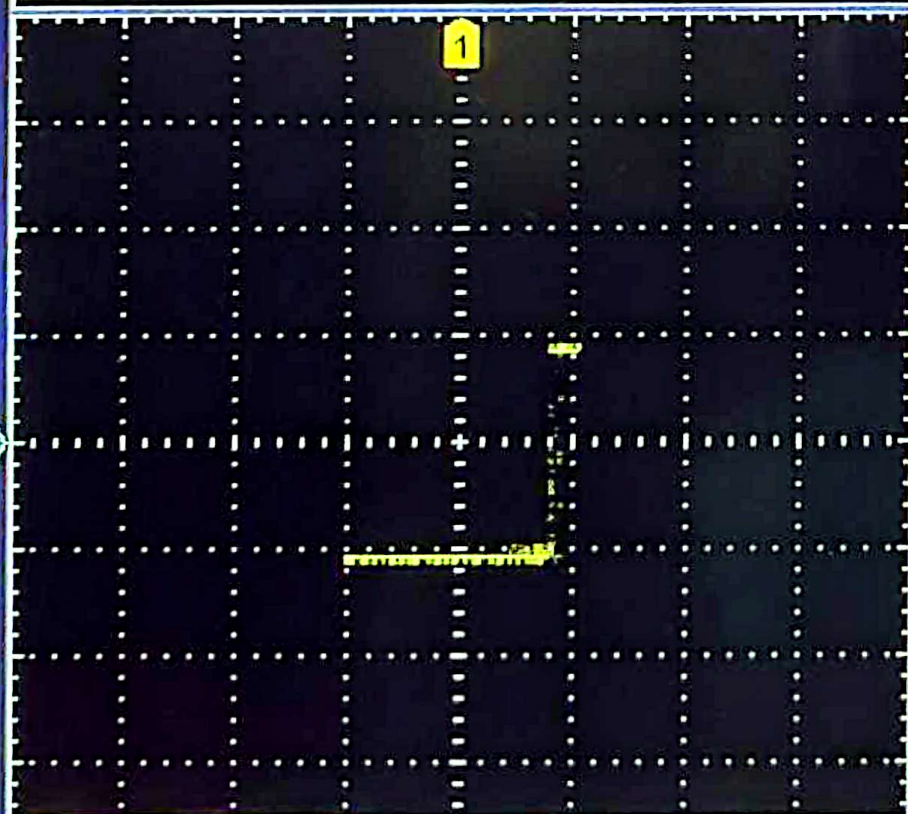

1 = 5.00V

2 = 10.0V

5ms

0.00000s

2

F

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center

XY

OFF(YT)

Triggered
XY

GWINSTEK


10k pts

200kSa/s




Trig'd

1

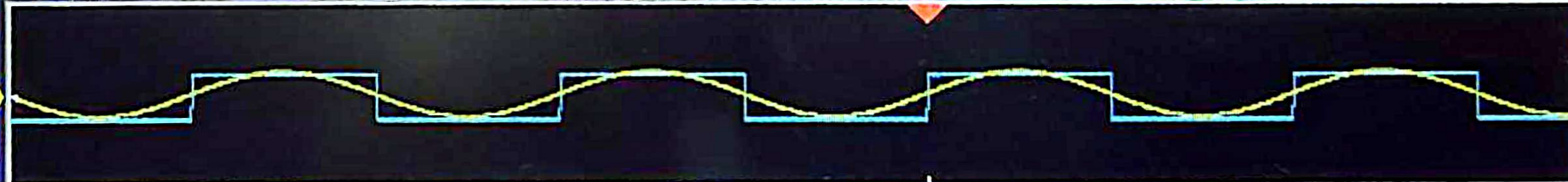

1

2

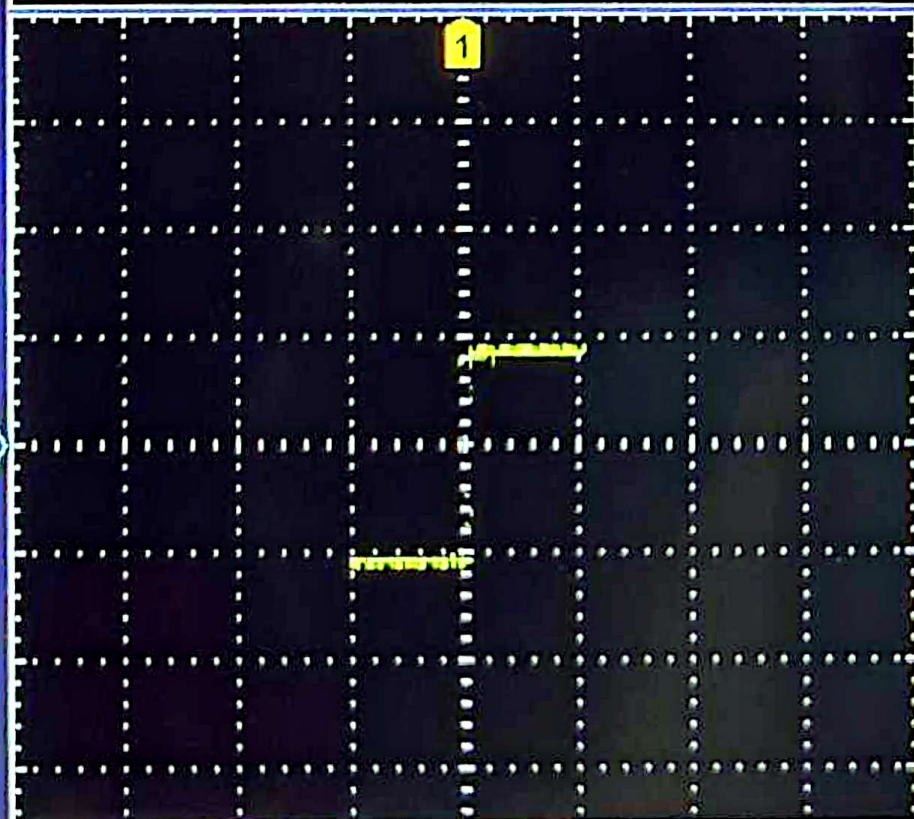

1 = 5.00V 2 = 10.0V

5ns

0.00000s

2

F

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center


XY

OFF(YT)

Triggered
XY

① Measurement Summary

Pk-Pk	9.80V	Frequency	100.0Hz
Max	5.00V	Period	10.00ms
Min	-4.80V	RiseTime	2.846ms
Amplitude	9.60V	FallTime	2.987ms
High	5.00V	+Width	5.050ms
Low	-4.60V	-Width	4.950ms
Mean	172mV	Dutycycle	50.50%
CycleMean	170mV	+Pulses	4
RMS	3.47V	-Pulses	5
CycleRMS	3.47V	+Edges	5
Area	8.62mVs	-Edges	4
CycleArea	1.70mVs		
ROVShoot	0.00%		
FOVShoot	2.08%		
RPREShoot	2.08%		
FPREShoot	0.00%		

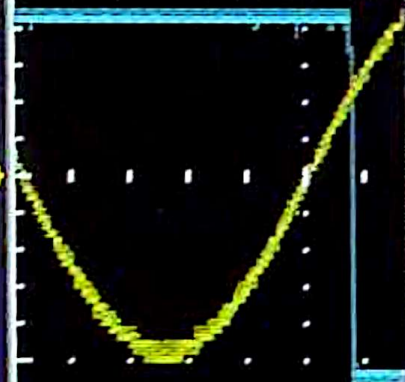

GWINSTEK


10k pts

200kSa/s




Trig'd

1

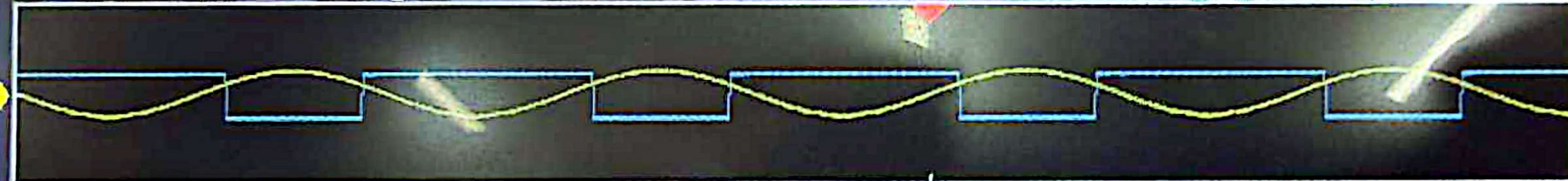

1

2

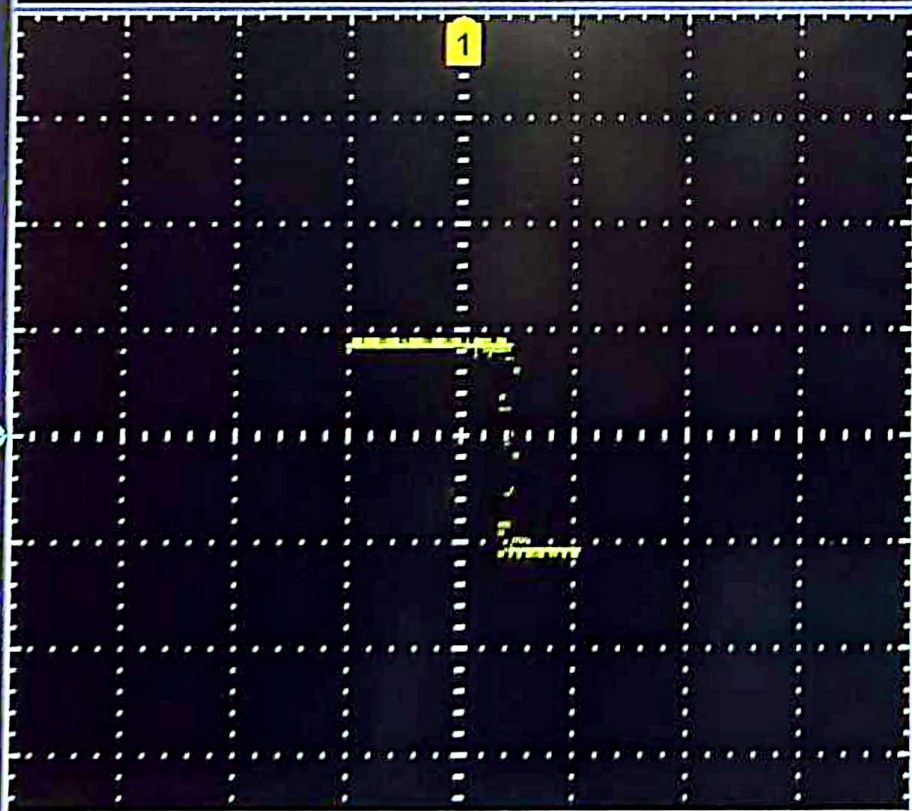

1 = 5.00V

2 = 10.0V

5ms

0.00000s

1

F

XY

OFF(YT)

Triggered
XY

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center

GWINSTEK


10k pts

200kSa/s




Trig'd

1

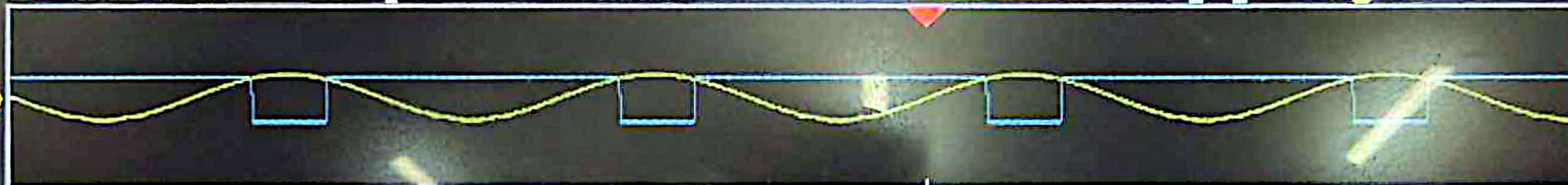

1

2

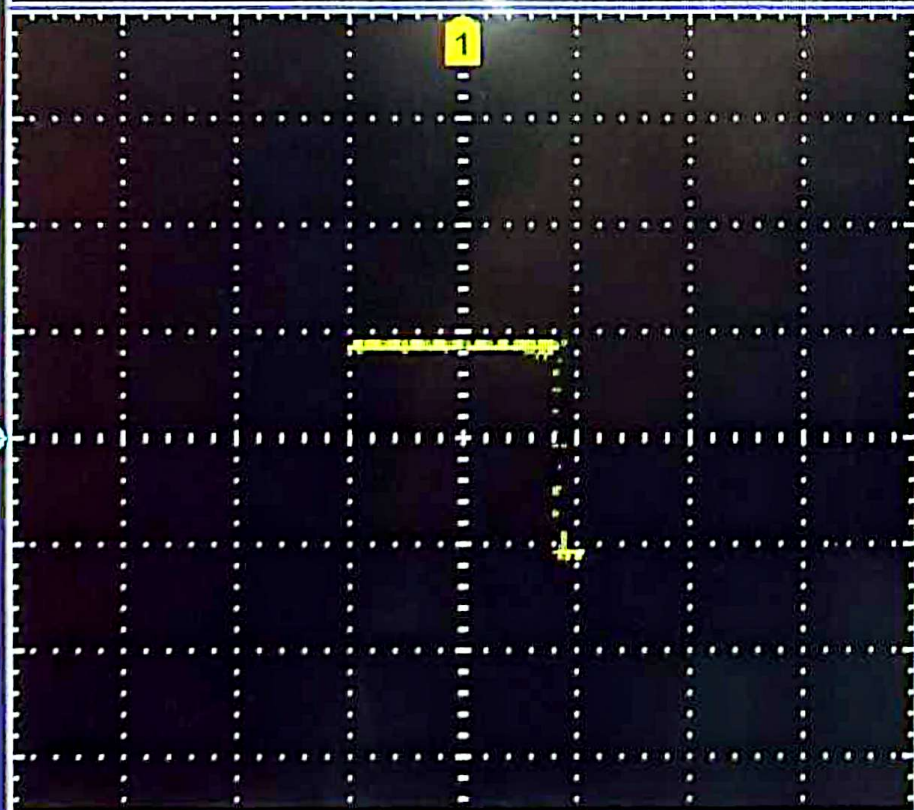

1 = 5.00V

2 = 10.0V

5ms

0.00000s

1

F

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center

XY

OFF(YT)

Triggered
XY

GWINSTEK


10k pts

200kSa/s




Trig'd

1

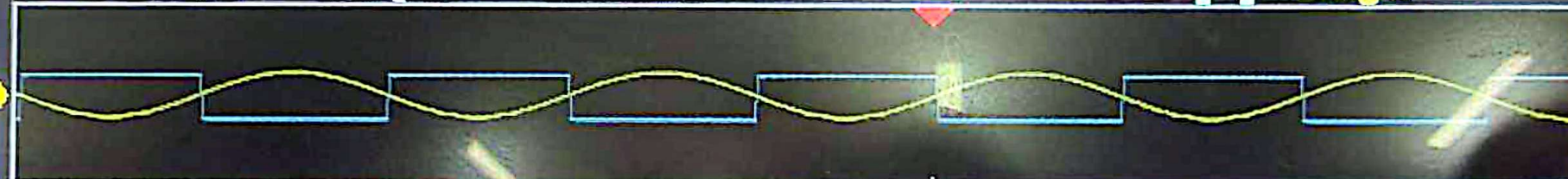

1

2

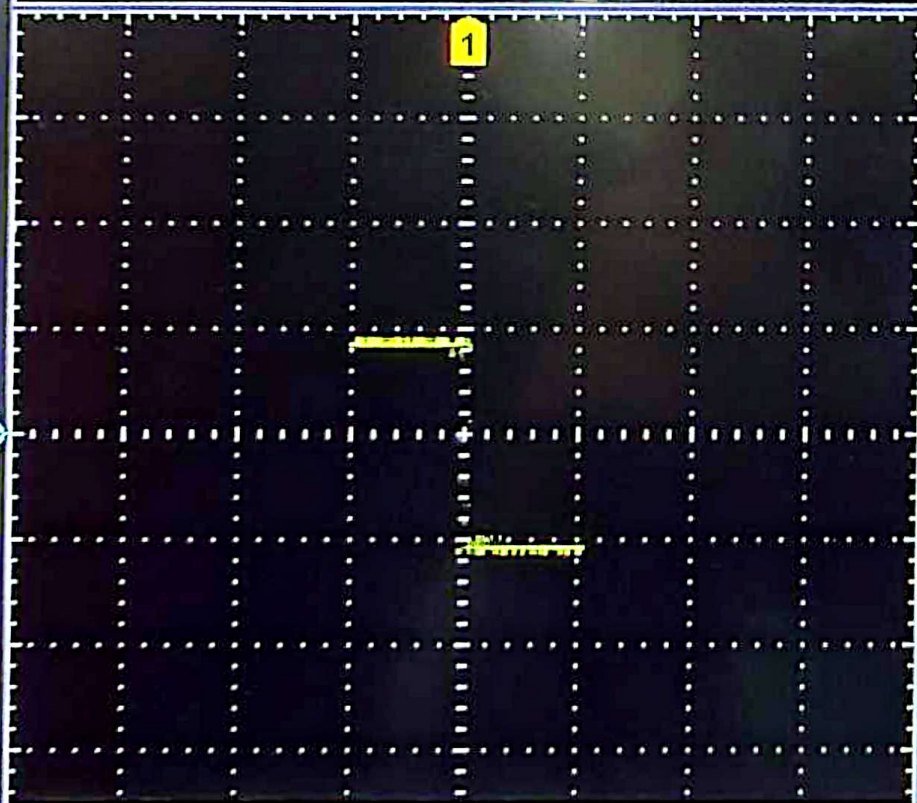

1 = 5.00V

2 = 10.0V

5ns

0.00000s

1

F

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center

XY

OFF(YT)

Triggered
XY


GWINSTEK

10k pts

200kSa/s



Trig'd

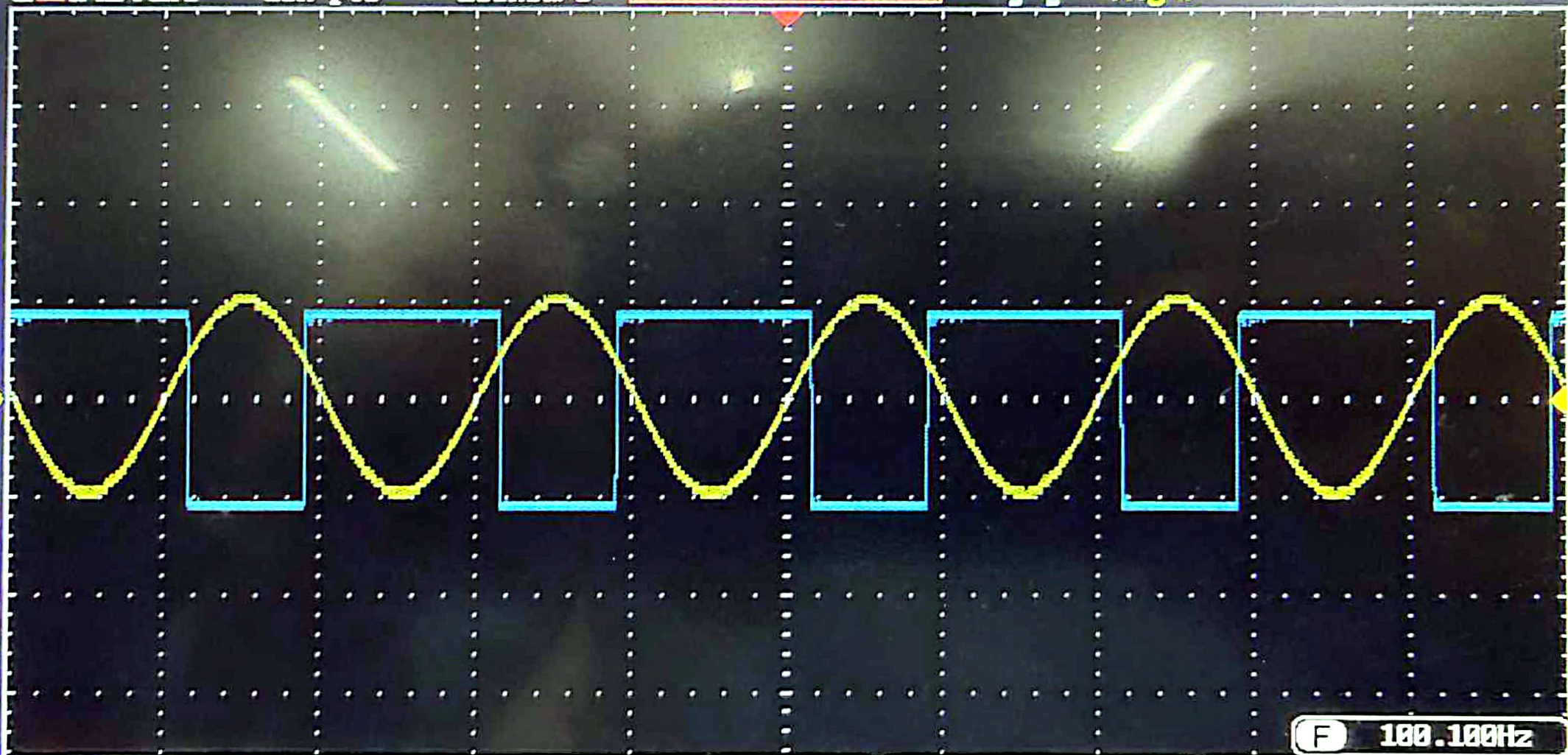

① = 5.00V ② = 10.0V

5ms

0.00000s



0V

DC

Mode
Fit Screen
AC Priority

Undo
Autoset

GWINSTEK

10k pts

200kSa/s



Trig'd

① Measurement Summary

Pk-Pk	2.08V	Frequency	100.3Hz
Max	1.12V	Period	9.975ms
Min	-960mV	RiseTime	2.870ms
Amplitude	2.00V	FallTime	3.090ms
High	1.04V	+Width	5.170ms
Low	-960mV	-Width	4.805ms
Mean	60.3mV	Dutycycle	51.83%
CycleMean	59.3mV	+Pulses	4
RMS	722mV	-Pulses	5
CycleRMS	723mV	+Edges	5
Area	3.01mVs	-Edges	4
CycleArea	592uVs		
ROVShoot	4.00%		
FOVShoot	0.00%		
RPREShoot	0.00%		
FPREShoot	4.00%		

CH1

CH2

Math

Display All

Source

CH1

OFF

① = 2.00V ② = 2.00V

5ms 0.00000s

① ↕

Add
MeasurementRemove
MeasurementGating
ScreenDisplay All
CH1High-Low
Auto

Statistics

Reference
Levels

GWINSTEK

10k pts

200kSa/s



Trig'd

Display All

② Measurement Summary

Pk-Pk	7.92V	Frequency	100.1Hz
Max	4.16V	Period	9.990ms
Min	-3.76V	RiseTime	2.958ms
Amplitude	7.76V	FallTime	2.973ms
High	4.08V	+Width	5.035ms
Low	-3.68V	-Width	4.955ms
Mean	228mV	Dutycycle	50.40%
CycleMean	227mV	+Pulses	4
RMS	2.75V	-Pulses	5
CycleRMS	2.75V	+Edges	5
Area	11.4mVs	-Edges	4
CycleArea	2.27mVs		
ROVShoot	1.03%		
FOVShoot	1.03%		
RPREShoot	1.03%		
FPREShoot	1.03%		

CH1

CH2

Math

Source

CH2

OFF

① = 2.00V

② = 2.00V

5ms

0.00000s

①

↑

Add
MeasurementRemove
MeasurementGating
ScreenDisplay All
CH2High-Low
Auto

Statistics

Reference
Levels


GWINSTEK

10k pts

200kSa/s



Trig'd

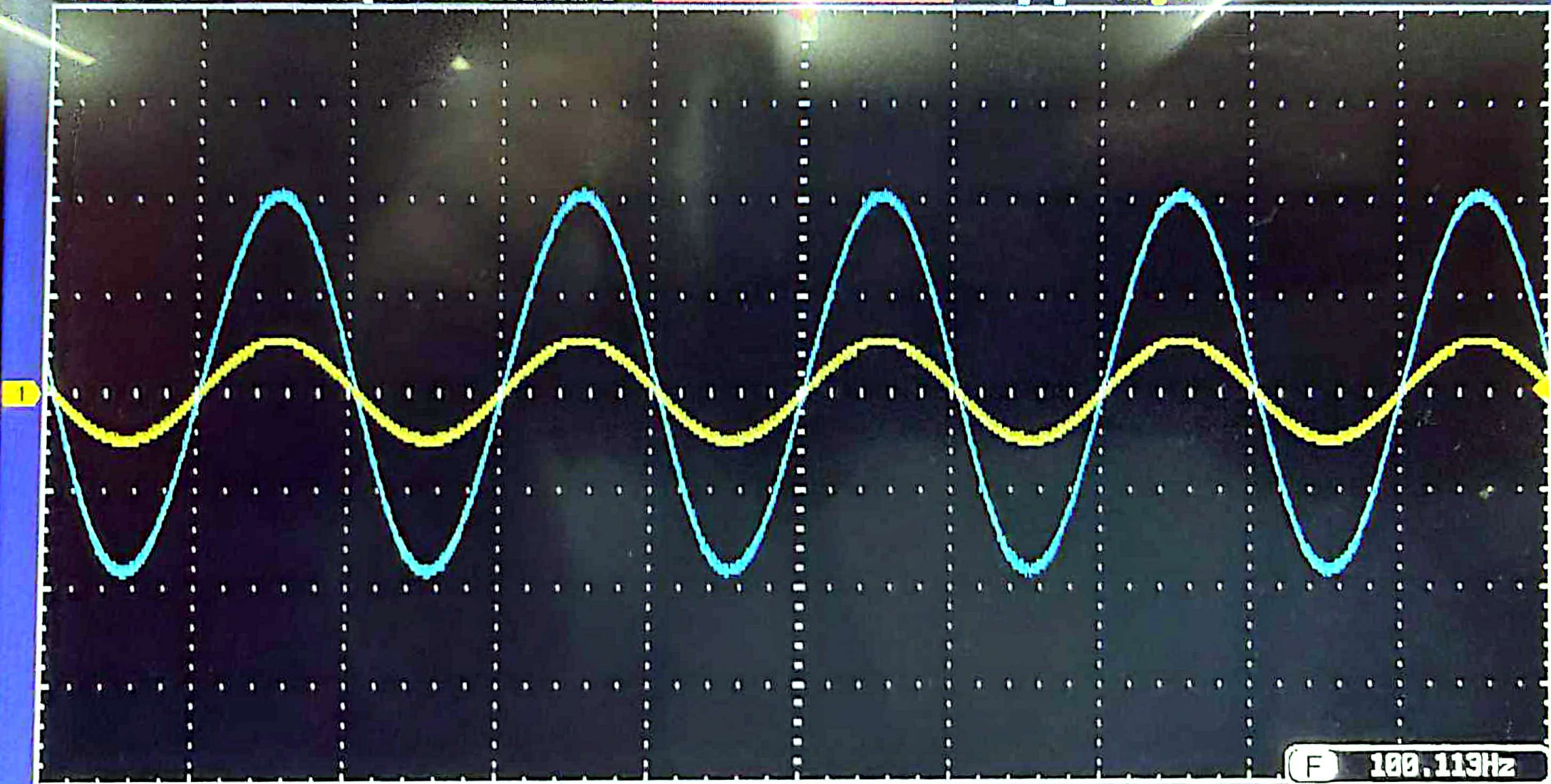

1

2.00V

2

2.00V

5ns

0.00000s

F

100.113Hz

80mV

DC

GWINSTEK


10k pts

200kSa/s




Trig'd

1

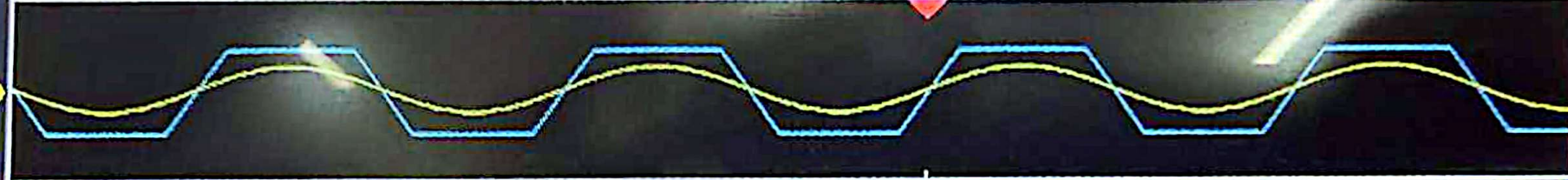

2

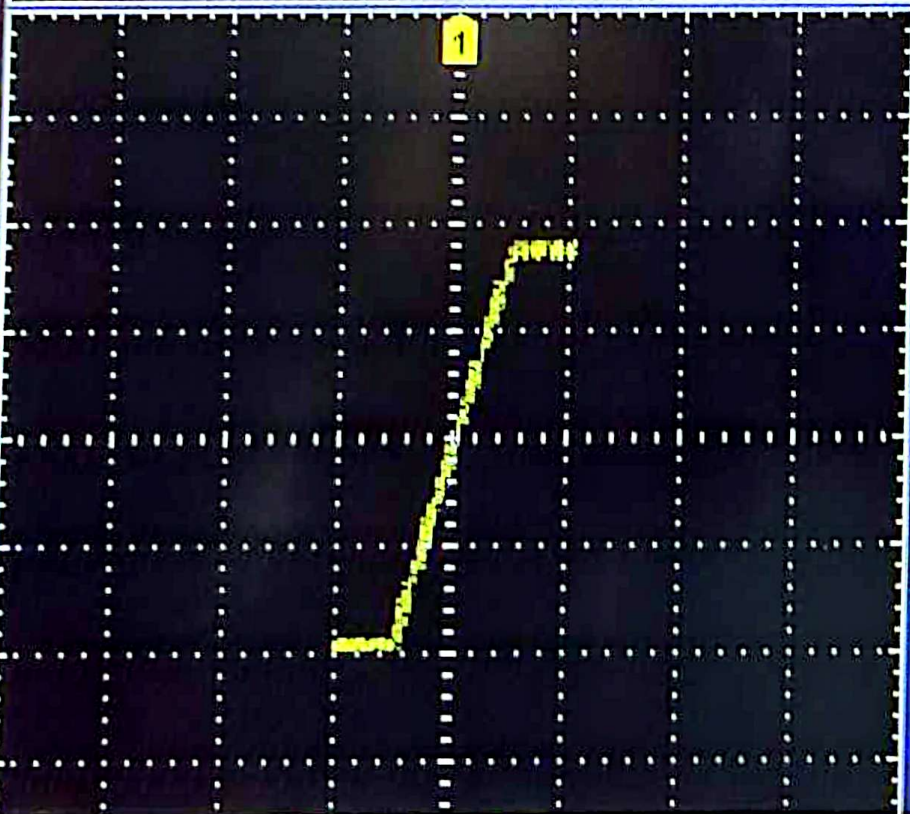

1 = 5.00V 2 = 5.00V

5ms 0.00000s

1 f

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center

XY

OFF(YT)

Triggered
XY

GWINSTEK


10k pts

2MSa/s



Trig'd

1

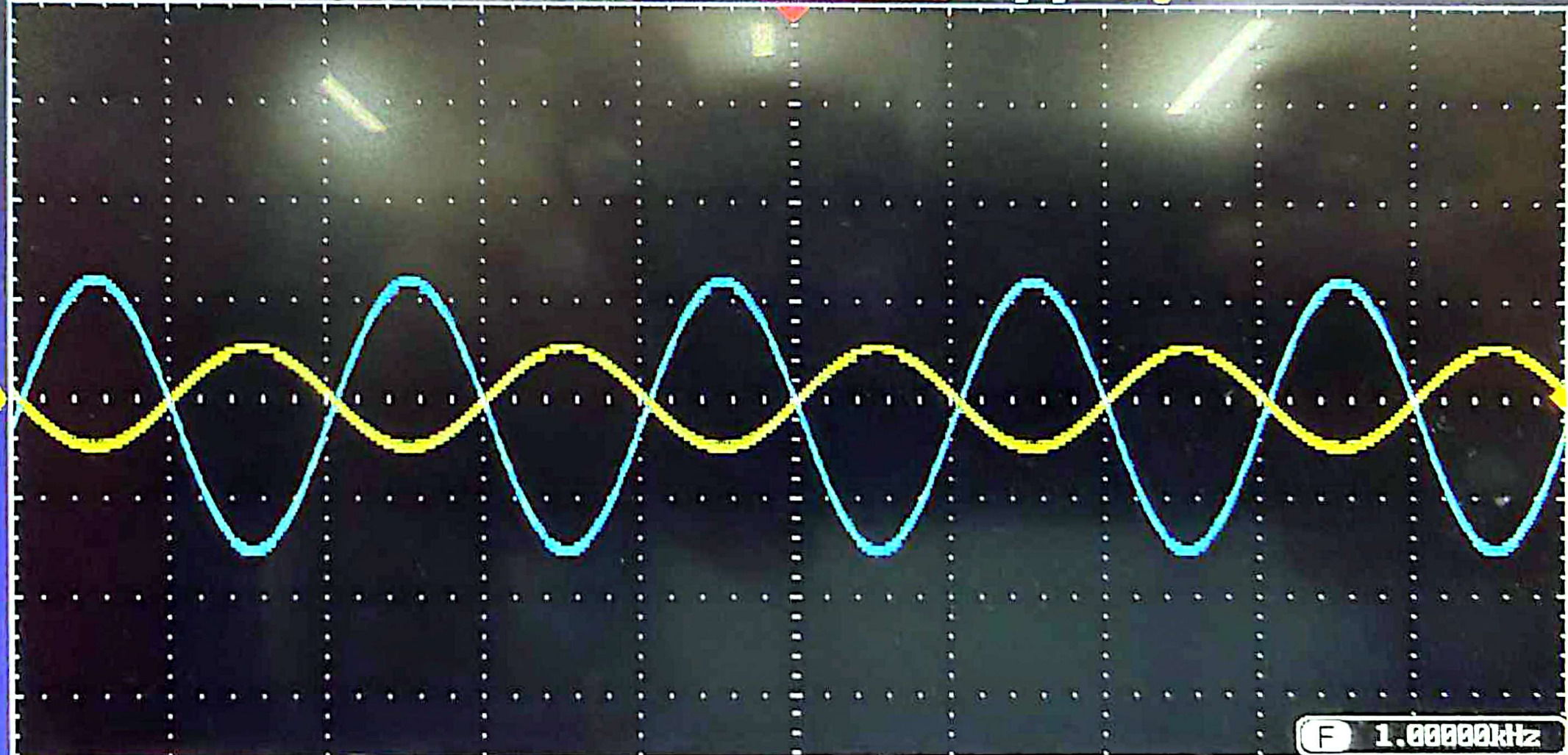

① = 2.00V ② = 2.00V

500us

0.00000s

F 1.00000kHz

① 80mV

DC

Mode
Fit Screen
AC Priority

Undo
Autoset

GWINSTEK

10k pts

2MSa/s



Trig'd

② Measurement Summary

Pk-Pk	5.52V	Frequency	999.5Hz
Max	2.40V	Period	1.000ms
Min	-3.12V	RiseTime	291.3us
Amplitude	5.36V	FallTime	284.8us
High	2.32V	+Width	510.1us
Low	-3.04V	-Width	490.3us
Mean	-316mV	Dutycycle	50.99%
CycleMean	-316mV	+Pulses	5
RMS	1.95V	-Pulses	4
CycleRMS	1.95V	+Edges	4
Area	-1.58mVs	-Edges	5
CycleArea	-316uVs		
ROVShoot	1.49%		
FOVShoot	1.49%		
RPRESshoot	1.49%		
FPRESshoot	1.49%		

CH1

CH2

Math

Display All

Source

CH2

OFF

① == 2.00V ② == 2.00V

500us 0.00000s

① ↑

Add
MeasurementRemove
MeasurementGating
ScreenDisplay All
CH2High-Low
Auto

Statistics

Reference
Levels

GWINSTEK

10k pts

2MSa/s



Trig'd

Display All

① Measurement Summary

Pk-Pk	2.00V	Frequency	999.5Hz
Max	1.04V	Period	1.000ms
Min	-960mV	RiseTime	284.6us
Amplitude	1.92V	FallTime	294.1us
High	1.04V	+Width	493.0us
Low	-880mV	-Width	507.5us
Mean	52.1mV	Dutycycle	49.28%
CycleMean	52.5mV	+Pulses	4
RMS	700mV	-Pulses	4
CycleRMS	699mV	+Edges	5
Area	260uVs	-Edges	4
CycleArea	52.6uVs		
ROVShoot	0.00%		
FOVShoot	4.17%		
RPRESshoot	4.17%		
FPRESshoot	0.00%		

CH1

CH2

Math

Source

CH1

OFF

① = 2.00V ② = 2.00V

500us 0.00000s

① ↑

Add
MeasurementRemove
MeasurementGating
ScreenDisplay All
CH1High-Low
Auto

Statistics

Reference
Levels

GWINSTEK

10k pts

2MSa/s

Trig'd

Trig'd

1

1

2

XY

OFF(YT)

Triggered
XY

1 = 2.00V

2 = 2.00V

500us

0.00000s

1

F

Mode
Sample

Reset H
Position to 0s

XY

Record Length
10k

Expand
By Center