

Student ID:	24301500	Lab Section:	7B
Name:	Masidul Islam Kabbo	Lab Group:	6

Experiment-04

Study of Half-Wave and Full-Wave Rectifier

CSE251 - Electronic Devices and Circuits Lab



Inspiring Excellence

Objective

1. To build a half-wave rectifier circuit and understand its operating principle.
2. To build a full-wave rectifier circuit and understand its operating principle.

Equipments

1. p-n junction diode (1N4007) x 4
2. Resistor ($10k\Omega$) - x1
3. Capacitors ($1\mu F$, $4.7\mu F$) - 1 each
4. Function Generator
5. Oscilloscope
6. Multimeter
7. Breadboard and Wires

Background Theory

Diodes are used to build rectifier circuits which convert the input sinusoidal voltage V_s to a unipolar output V_o . There are two types of rectifier circuits: (i) Half-wave rectifier and (ii) Full-wave rectifier.

Half-Wave (HW) Rectifier

The circuit of a half-wave rectifier is shown in the following figure:

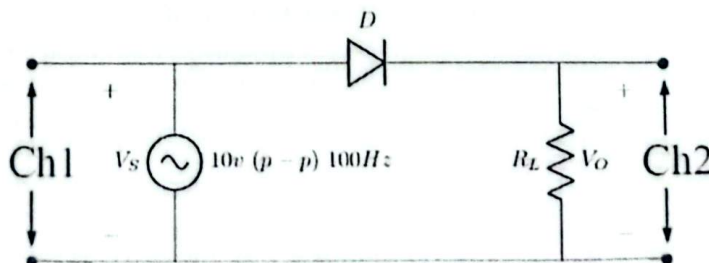


Figure 1: *Half-Wave Rectifier*

Assuming ideal diode model,

For the period, $t = 0 \rightarrow T/2$, $V_s > 0$, Diode is ON and $V_o = V_s$

For the period, $t = T/2 \rightarrow T$, $V_s < 0$, Diode is OFF and $V_o = 0$

As only positive half cycle appears at the output and the negative half is blocked, the AC input voltage changes into a unidirectional DC voltage at the output. The process of removing half of the input signal to establish a dc level is aptly called half-wave rectification. Due to diode voltage drop, the actual output voltage will be

Data Sheet

Experimental Observation: HW Rectifier

$$V_{in\ max} = 5.04$$

1. HW Rectifier without Capacitor:

$$\text{Diode voltage, } V_{D0} = \text{Input}_{\max} (\text{oscilloscope}) - \text{Output}_{\max} (\text{oscilloscope}) = 0.56$$

$$\text{Maximum output voltage, } V_p (\text{oscilloscope}) = 4.48V$$

$$\text{Average or DC output voltage, } V_{dc} (\text{multimeter in DC mode}) = 1.368$$

$$\text{RMS or AC output voltage, } V_{r-rms} (\text{multimeter in AC mode}) = 1.725$$

2. HW Rectifier with $1\mu F$ Capacitor:

$$\text{Diode voltage, } V_{D0} = \text{Input}_{\max} (\text{oscilloscope}) - \text{Output}_{\max} (\text{oscilloscope}) = 0.48$$

$$\text{Maximum output voltage, } V_p (\text{oscilloscope}) = 4.56$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)} (\text{oscilloscope}) = 2.64$$

$$\text{Average or DC value of the ripple voltage, } V_{dc} (\text{multimeter in DC mode}) = 3.173$$

$$\text{RMS or AC value of the ripple voltage, } V_{r-rms} (\text{multimeter in AC mode}) = 0.740$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.233$$

3. HW Rectifier with $4.7\mu F$ Capacitor:

$$\text{Diode voltage, } V_{D0} = \text{Input}_{\max} (\text{oscilloscope}) - \text{Output}_{\max} (\text{oscilloscope}) = 0.72$$

$$\text{Maximum output voltage, } V_p (\text{oscilloscope}) = 4.32$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)} (\text{oscilloscope}) = 0.88$$

$$\text{Average or DC value of the ripple voltage, } V_{dc} (\text{multimeter in DC mode}) = 3.97$$

$$\text{RMS or AC value of the ripple voltage, } V_{r-rms} (\text{multimeter in AC mode}) = 0.216$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.054$$

Theoretical Calculation: HW Rectifier

1. HW Rectifier Without Capacitor:

$$\text{Maximum output voltage, } V_p (\text{see the experimental observation}) = 4.48V$$

$$\text{Maximum input voltage, } V_m = 5.04V$$

$$\text{Diode voltage, } V_{D0} (\text{see the experimental observation}) = 0.56V$$

$$\text{DC output voltage of the rectifier, } V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2} = 1.32V$$

$$\text{RMS or AC output voltage, } V_{r-rms} = \frac{V_p}{2} = 2.24V$$

2. HW Rectifier With $1\mu F$ Capacitor:

$$\text{Maximum output voltage, } V_p (\text{see the experimental observation}) = 4.56$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)} (\text{see the experimental observation}) = 2.64$$

$$\text{DC value of the ripple voltage, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.24$$

$$\text{RMS value of the ripple voltage, } V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.762$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.235$$

3. HW Rectifier with $4.7\mu F$ Capacitor:

$$\text{Maximum output voltage, } V_p (\text{see the experimental observation}) = 4.32$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)} (\text{see the experimental observation}) = 0.88$$

$$\text{DC value of the ripple voltage, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.88$$

$$\text{RMS value of the ripple voltage, } V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.254$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.0654$$

Experimental Observation: FW Rectifier

1. FW Rectifier without Capacitor:

$$\text{Diode voltage, } V_{D0} = \frac{\text{Input}_{\max}(\text{oscilloscope}) - \text{Output}_{\max}(\text{oscilloscope})}{2} = 0.56$$

$$\text{Maximum output voltage, } V_p(\text{oscilloscope}) = 3.92$$

$$\text{Average or DC output voltage, } V_{dc}(\text{multimeter in DC mode}) = 2.224$$

$$\text{RMS or AC output voltage, } V_{r-rms}(\text{multimeter in AC mode}) = 1.341$$

2. FW Rectifier with $1\mu\text{F}$ Capacitor:

$$\text{Diode voltage, } V_{D0} = \frac{\text{Input}_{\max}(\text{oscilloscope}) - \text{Output}_{\max}(\text{oscilloscope})}{2} = 0.55$$

$$\text{Maximum output voltage, } V_p(\text{oscilloscope}) = 3.94$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)}(\text{oscilloscope}) = 1.22$$

$$\text{Average or DC value of the ripple voltage, } V_{dc}(\text{multimeter in DC mode}) = 3.325$$

$$\text{RMS or AC value of the ripple voltage, } V_{r-rms}(\text{multimeter in AC mode}) = 0.348$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.104$$

3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:

$$\text{Diode voltage, } V_{D0} = \frac{\text{Input}_{\max}(\text{oscilloscope}) - \text{Output}_{\max}(\text{oscilloscope})}{2} = 0.61$$

$$\text{Maximum output voltage, } V_p(\text{oscilloscope}) = 3.82$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)}(\text{oscilloscope}) = 0.4$$

$$\text{Average or DC value of the ripple voltage, } V_{dc}(\text{multimeter in DC mode}) = 3.591$$

$$\text{RMS or AC value of the ripple voltage, } V_{r-rms}(\text{multimeter in AC mode}) = 0.091$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.025$$

Theoretical Calculation: FW Rectifier

1. FW Rectifier without Capacitor:

$$\text{Maximum output voltage, } V_p(\text{see the experimental observation}) = 3.92$$

$$\text{Maximum input voltage, } V_m = 5.04$$

$$\text{Diode voltage, } V_{D0}(\text{see the experimental observation}) = 0.56$$

$$\text{DC output voltage of the rectifier, } V_{dc} = \frac{2V_m}{\pi} - 2V_{D0} = 2.088$$

$$\text{RMS or AC output voltage, } V_{r-rms} = \frac{V_p}{\sqrt{2}} = 2.77$$

2. FW Rectifier with $1\mu\text{F}$ Capacitor:

$$\text{Maximum output voltage, } V_p(\text{see the experimental observation}) = 3.94$$

$$\text{Peak to peak ripple voltage, } V_{r(p-p)}(\text{see the experimental observation}) = 1.22$$

$$\text{DC value of the ripple voltage, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.33$$

$$\text{RMS value of the ripple voltage, } V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.3521$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.106$$

3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:

$$\text{Maximum output voltage, } V_p(\text{see the experimental observation}) = 3.82$$

$$\text{Peak to peak ripple voltage, } V_p(\text{see the experimental observation}) = 0.4$$


$$\text{DC value of the ripple voltage, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.62$$

$$\text{RMS value of the ripple voltage, } V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.11$$

$$\text{Ripple factor, } r = V_{r-rms}/V_{dc} = 0.032$$

Table for Comparison

	C(μF)	Experimental Observation			Theoretical Calculation		
		V_{r-rms} (V)	V_{dc} (V)	Ripple Factor, r	V_{r-rms} (V)	V_{dc} (V)	Ripple Factor, r
HW	1	0.74	3.173	0.233	0.762	3.24	0.235
	4.7	0.216	3.92	0.054	0.254	3.88	0.0654
FW	1	0.348	3.325	0.104	0.3521	3.33	0.106
	4.7	0.091	3.591	0.025	0.11	3.62	0.032

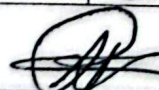 3-12-2023
Signature of the lab faculty

Report Submission Guidelines

1. Attach the signed Data Sheet (if any)
2. Attach the captured images (if any)
3. Answer the questions in the "Test Your Understanding" section
4. Add a brief Discussion regarding the experiment. For the Discussion part of the lab report, you should include the answers of the following questions in your own words:
 - What did you learn from this experiment?
 - What challenges did you face and how did you overcome the challenges? (if any)
 - What mistakes did you make and how did you correct the mistakes? (if any)
 - How will this experiment help you in future experiments of this course?

Test Your Understanding

Answer the following questions:

1. Which capacitor acts as a better filter? Explain briefly.

Answer:

4.7 μ F, it has a higher capacitance so more charge is stored so there is less ripple. and the voltage output remains more smooth. and the output is more stable.

2. Which of the two rectifiers is better? Which quantity is calculated for this purpose? Explain briefly.

Answer:

Full wave bridge rectifier is better as full wave gives two pulses per cycle, while half wave gives one.

More pulses give smoother output and there's less ripple.

We calculate ripple factor to know which rectifier is better,

we know $\gamma = \frac{V_{rms}}{V_{dc}}$, the higher the V_{dc} , the lower the γ the better the rectifier as less ripple. Full wave bridge has a lower γ .

3. Why can't you see the input and output using both channels of the oscilloscope simultaneously in Task-02?

Answer:


Both channels have their grounds internally shorted.

In full bridge rectifiers, the AC input has no ground reference and the DC output has its own ground after the diodes.

If both channels are connected, AC and DC reference points get shorted and one waveform would become noisy or disappear, as there is a ground conflict.

I learned about rectifiers in this experiment, mainly how to setup a full bridge rectifier. The instructions given for this experiment were clear and easy to understand, so I didn't face much of a challenge. The only mistake we made was we forgot to take a few measurements because we were going too fast so we had to redo the experiment to take those measurements. This experiment may help me construct a power supply from AC power source.

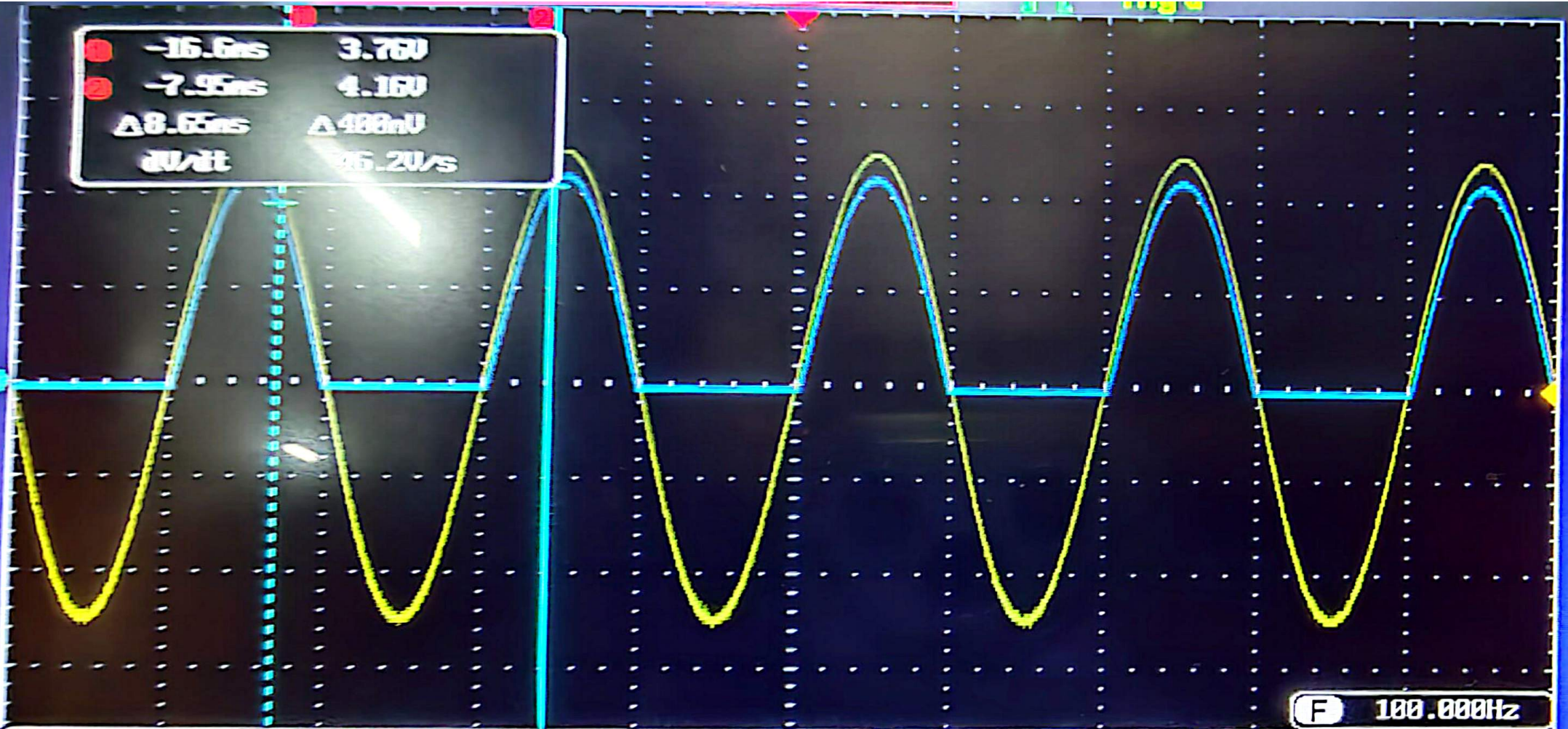1 -16.6ns 3.76V
2 -7.95ns 4.16V
 $\Delta 8.65ns$ $\Delta 488mV$
20V/div 25.20V/s



F 100.000Hz

● = 2.80V ● = 2.80V

5ms 0.00000s

1 f 0V DC

Mode
Fit Screen
AC Priority

Undo
Autoset

GWINSTEK


10k pts

200kSa/s



Trig'd

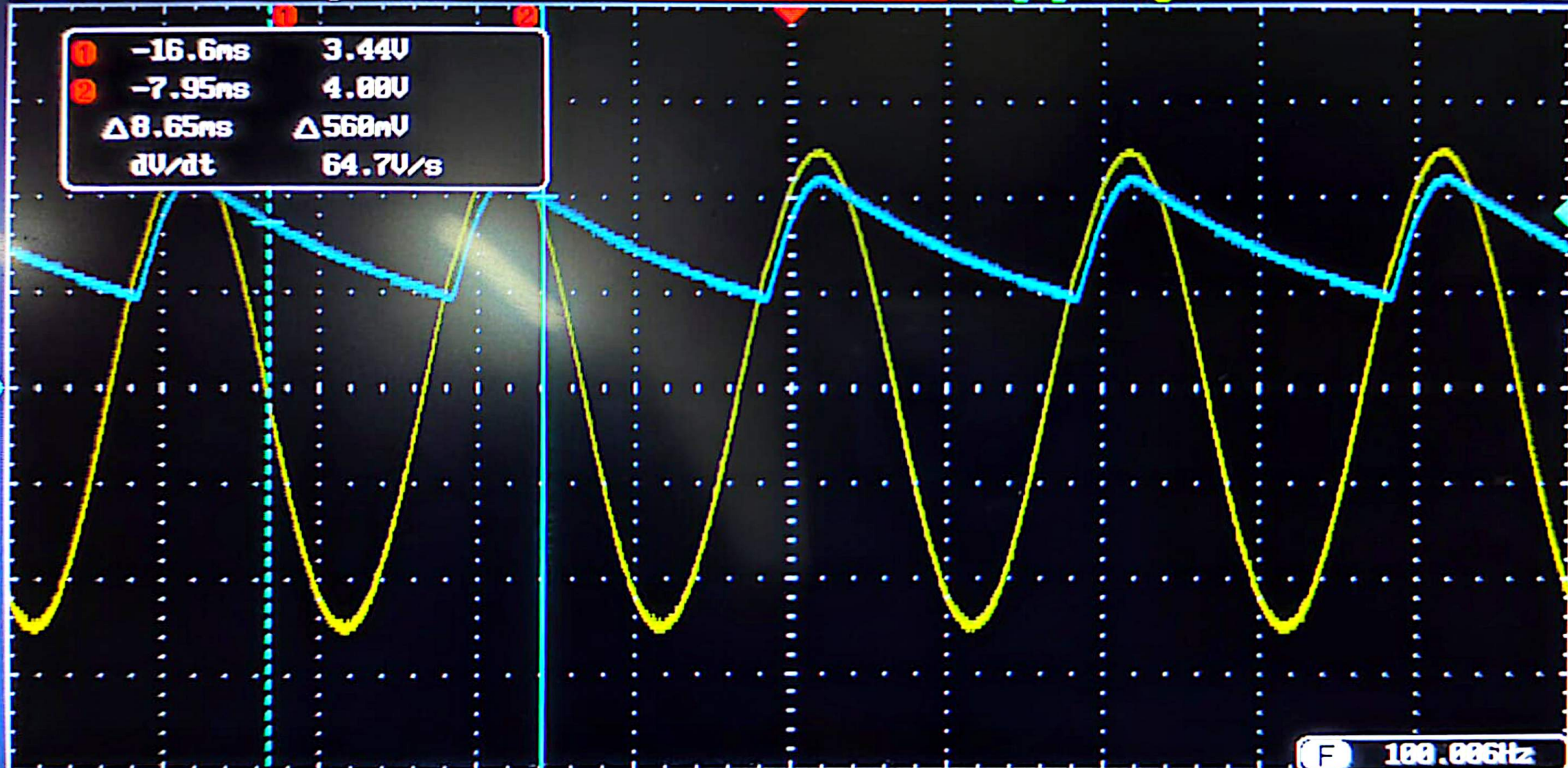① -16.6ns 3.44V
② -7.95ns 4.00V
 $\Delta 8.65\text{ns}$ $\Delta 568\text{nV}$
 dV/dt 64.7V/s



① = 2.00V ② = 2.00V

5ns

0.00000s

F 100.006Hz
② f 3.68V DC


INSTEK

10k pts

200kSa/s

Trig'd

①	-16.6ns	4.24V
②	-9.85ns	3.52V
	$\Delta 7.55\text{ns}$	$\Delta 720\text{mV}$
	dV/dt	-95.3V/s

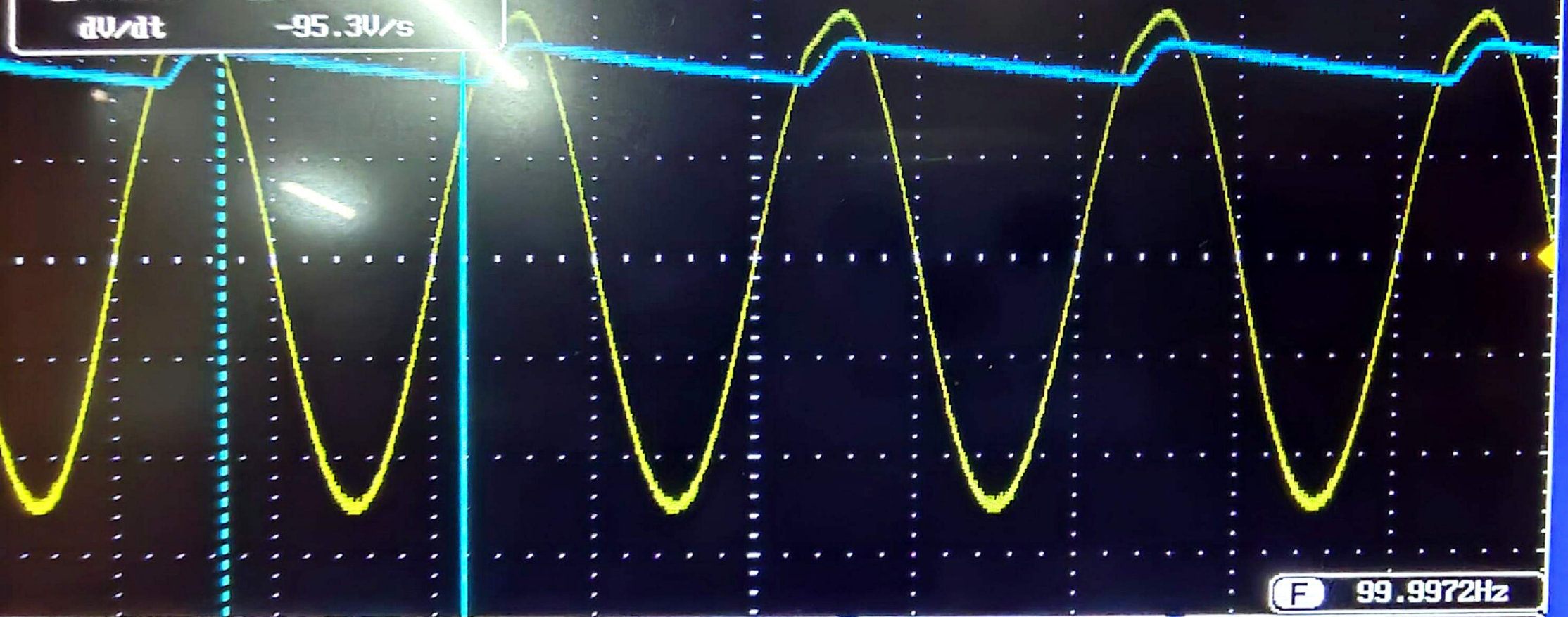

2.00V 2.00V

5ns

0.00000s

99.9972Hz

DC

GWINSTEK


10k pts

200kSa/s



Trig'd

①	-16.6ns	4.24V
②	-9.05ns	2.64V
$\Delta 7.55\text{ns}$		$\Delta 1.60\text{V}$
dV/dt		-211V/s

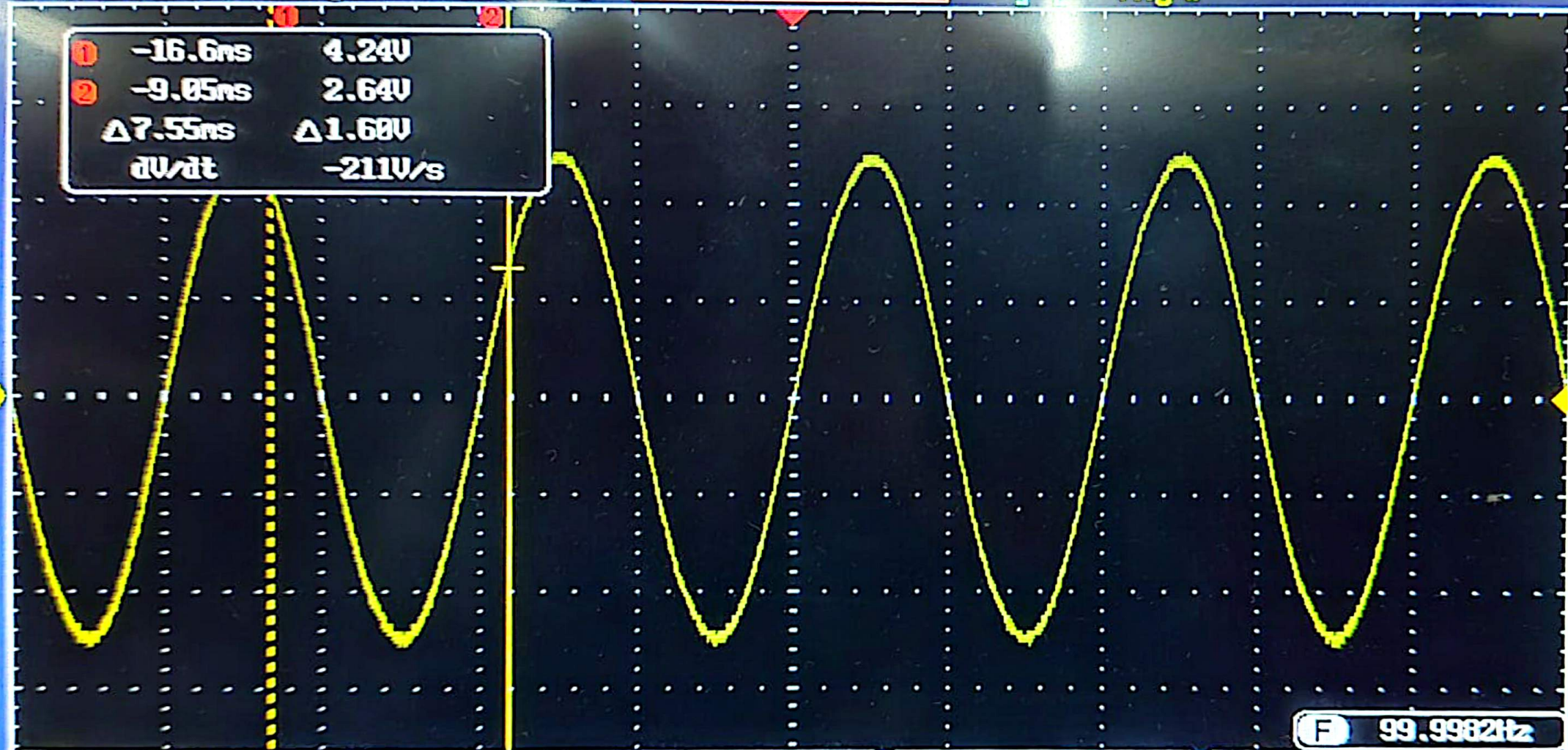

F 99.9982Hz

① = 2.00V ② = 2.00V

5ns

0.00000s

① 0V

DC

Mode
Fit Screen
AC Priority

Undo
Autoset

GWINSTEK


10k pts

500kSa/s



Trig'd

①	-6.64ns	3.12V
②	-3.62ns	3.76V
$\Delta 3.02\text{ns}$		$\Delta 640\text{mV}$
dV/dt		211V/s

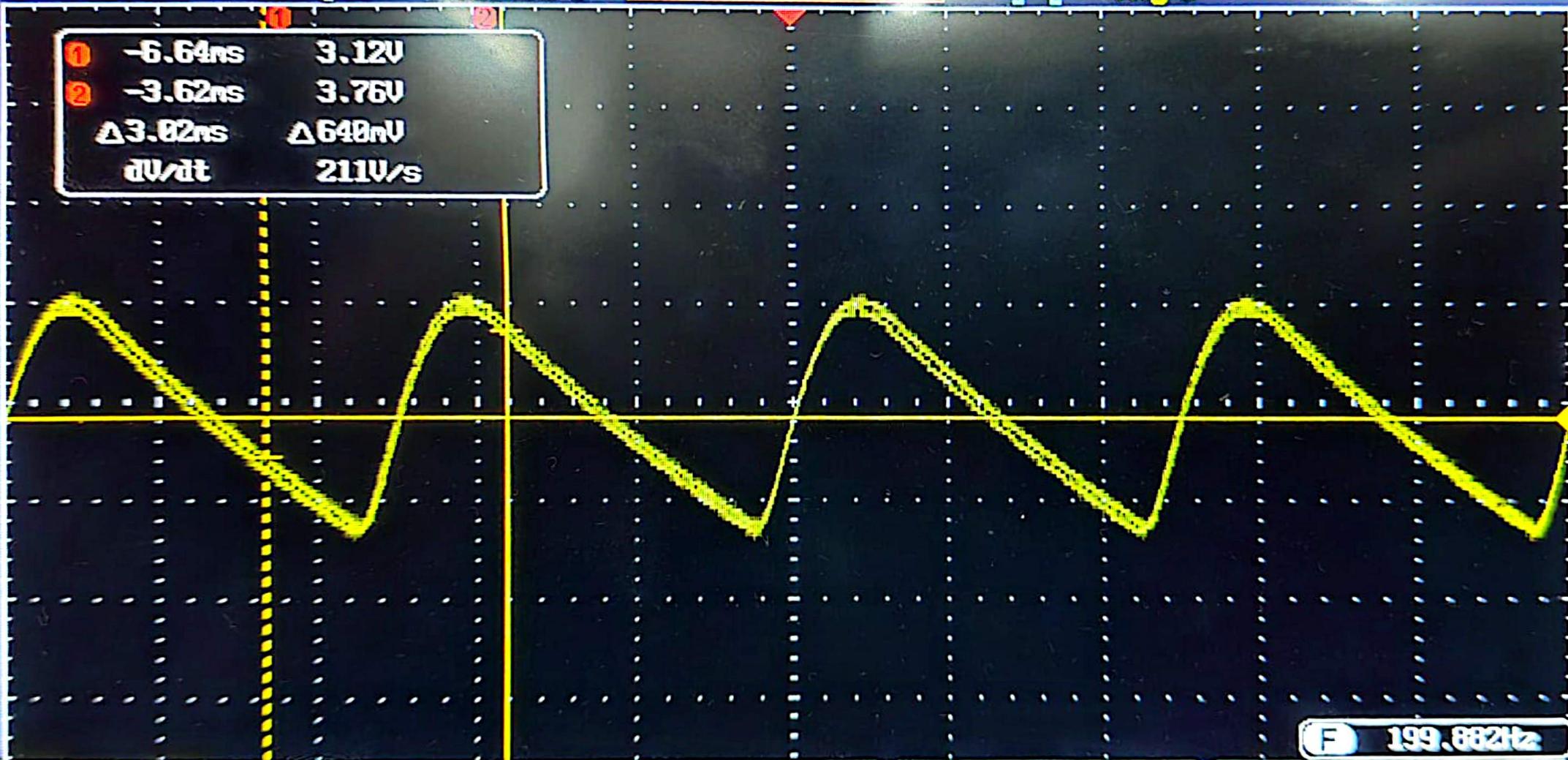

F 199.882Hz

① = 500mV ② = 2.00V

2ns

0.00000s

①

f

3.32V

DC

Mode
Fit Screen
AC PriorityUndo
Autoset

WINSTEK

10k pts

500kSa/s

Trig'd

①	-8.64ns	3.52V
②	-3.62ns	3.72V
$\Delta 3.02ns$		$\Delta 200mV$
dV/dt		66.2V/s



F 200.267Hz

2ns

0.00000s

1

3.76V

DC

Mode
Fit Screen
AC Priority

Undo
Autoset


WINSTEK

10k pts

500kSa/s

1mgV

①	-6.64ns	1.00V
②	-3.62ns	3.88V
	$\Delta 9.82ns$	$\Delta 2.88V$
	dV/dt	953V/s

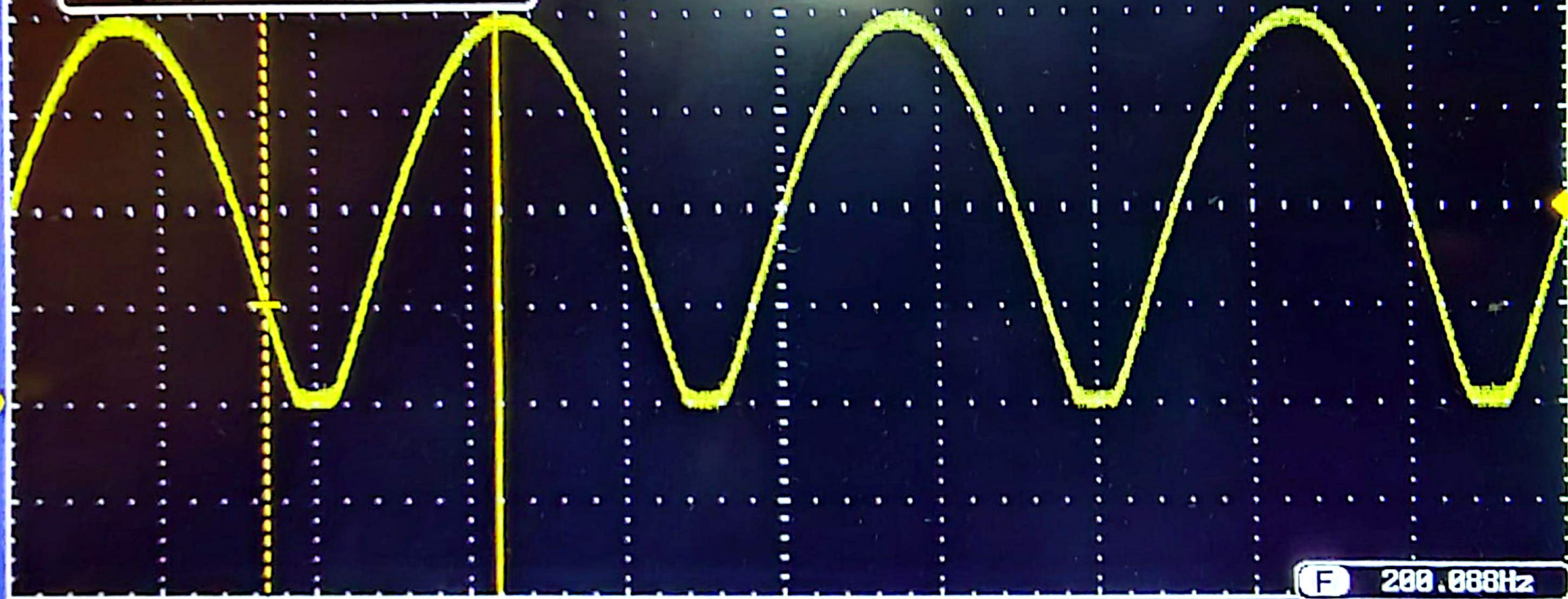

① = 1.00V ② = 2.00V

2ns 0.00000s

F 200.000Hz

① f 1.96V DC