


- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Proper units must be included for all calculated values. Marks will be deducted for missing or incorrect units.
- ✓ Symbols have their usual meanings.

■ Question 1 of 3

[CO2] [4 marks]

For the rectifier circuit shown, the diodes D_1 , D_2 , D_3 , and D_4 have cut-in voltages of 1.2 V, 0.5 V, 0.8 V, and 0.5 V, respectively. The input voltage v_S is a sinusoidal waveform as plotted below. Sketch the output voltage v_O on the same grid as v_S .

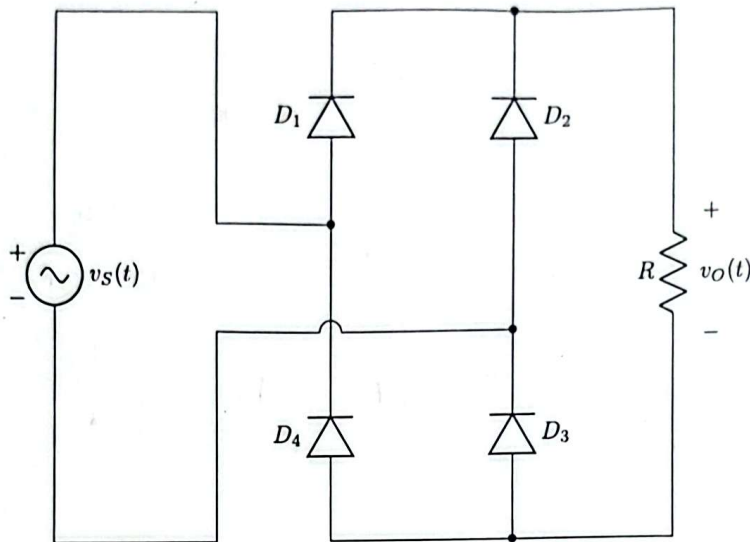
(-) half
cycles
 $D_2 \neq D_4$
ON
voltage
drop =
 $0.5 + 0.5$
 $= 1V$



(+) half cycles

$D_1 \neq D_3$
ON

Voltage drop
 $= 1.2 + 0.8$
 $= 2V$

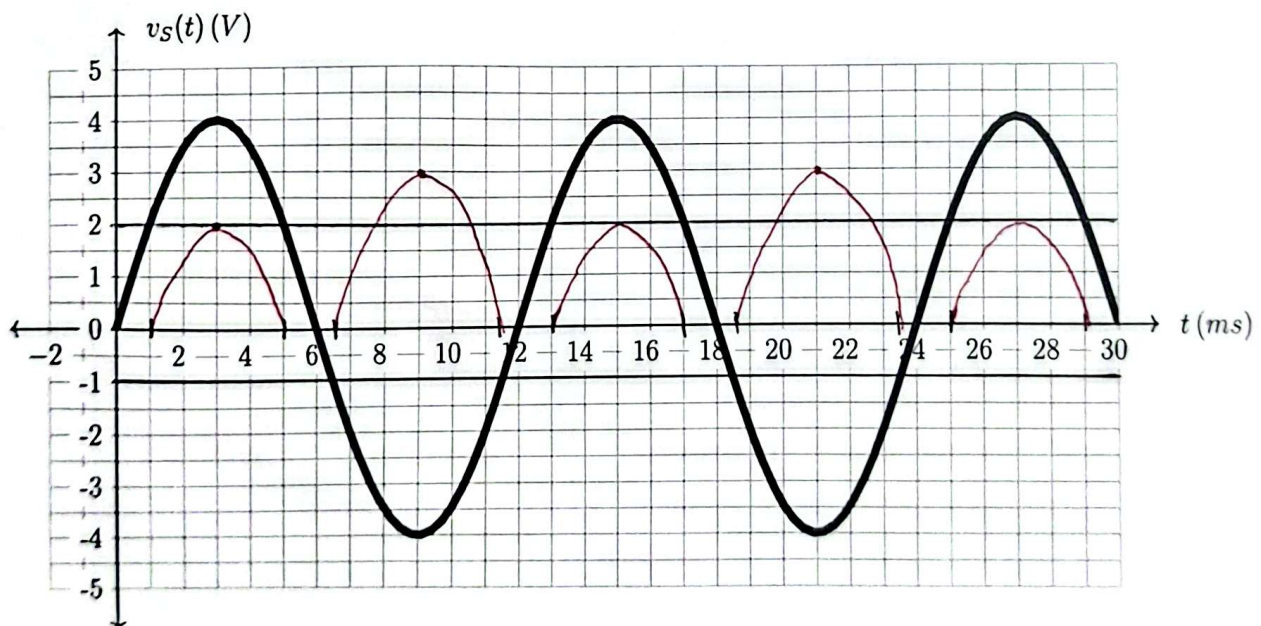

■ Question 2 of 3

[CO2] [6 marks]

A 12 V amplitude, 100 Hz sinusoidal AC voltage is rectified and filtered using a FW rectifier with 4 μ F filter capacitor. The diodes used in the rectifier are identical and have a cut-in voltage of 1.2 V. If the average output voltage is measured to be 9 V, determine the value of the load resistance.

$$V_m = 12 \text{ V}$$

$$f = 100 \text{ Hz}$$

$$C = 4 \times 10^{-6} \text{ F}$$

$$V_{D0} = 1.2 \text{ V}$$

$$V_{avg} = V_{DC} = 9 \text{ V}$$

$$V_p = V_m - 2V_{D0} = 9.6 \text{ V}$$

$$V_{avg} = V_p - \frac{V_r}{2}$$

$$\Rightarrow V_r = 2(V_p - V_{avg})$$
$$= 2(9.6 - 9) = 1.2 \text{ V}$$

$$V_r = \frac{V_p}{2fRC}$$


$$\Rightarrow 1.2 = \frac{9.6}{2 \times 100 \times R \times 4 \times 10^{-6}}$$

$$\Rightarrow \boxed{R = 10 \text{ k}\Omega}$$

■ Question 3 of 3

[CO3] [10 marks]

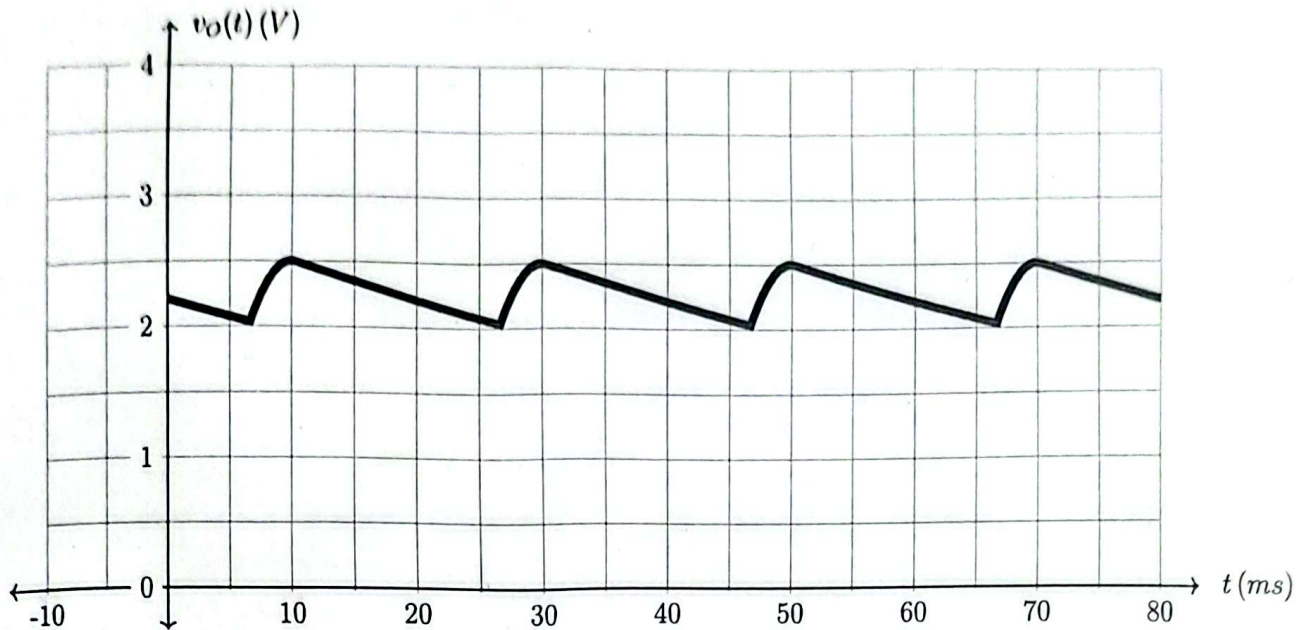The following is the rectified output of an AC sinusoidal voltage at 25 Hz frequency, applied to a load of $20\text{ k}\Omega$. The diode(s) used in the rectifier have a cut-in voltage of $V_{D0} = 0.6\text{ V}$.



- (a) [2 marks] What type of rectifier was used?
 (b) [4 marks] What is the filter capacitance value used in the rectifier design?
 (c) [2 marks] Write an expression for the input voltage as a function of time t .
 (d) [2 marks] Draw the circuit diagram of the rectifier.

(a) Time period of output = $30 - 10 = 20\text{ ms}$

Frequency of output = $\frac{1}{20\text{ ms}} = 50\text{ Hz}$

As output frequency = $2 \times$ Input frequency,

It was FW rectifier

(b) From the plot,

$$V_p = 2.5\text{ V}, V_r = 0.5\text{ V}$$

$$V_r = \frac{V_p}{2fRC}$$

$$\Rightarrow 0.5 = \frac{2.5}{2 \times 25 \times 20 \times 10^3 \times C} \Rightarrow \boxed{C = 5\text{ }\mu\text{F}}$$


$$\left. \begin{array}{l} f = 25\text{ Hz} \\ R = 20\text{ k}\Omega \\ V_{D0} = 0.6\text{ V} \end{array} \right\}$$

(c) $v_{in}(t) = V_m \sin(2\pi f t) \text{ (V)}$

$$V_m = V_p + 2V_{D_0} = 2.5 + 2 \times 0.6 \\ = 3.7 \text{ V}$$

$$v_{in}(t) = 3.7 \sin(2\pi 25 t) \text{ (V)}$$

(d)

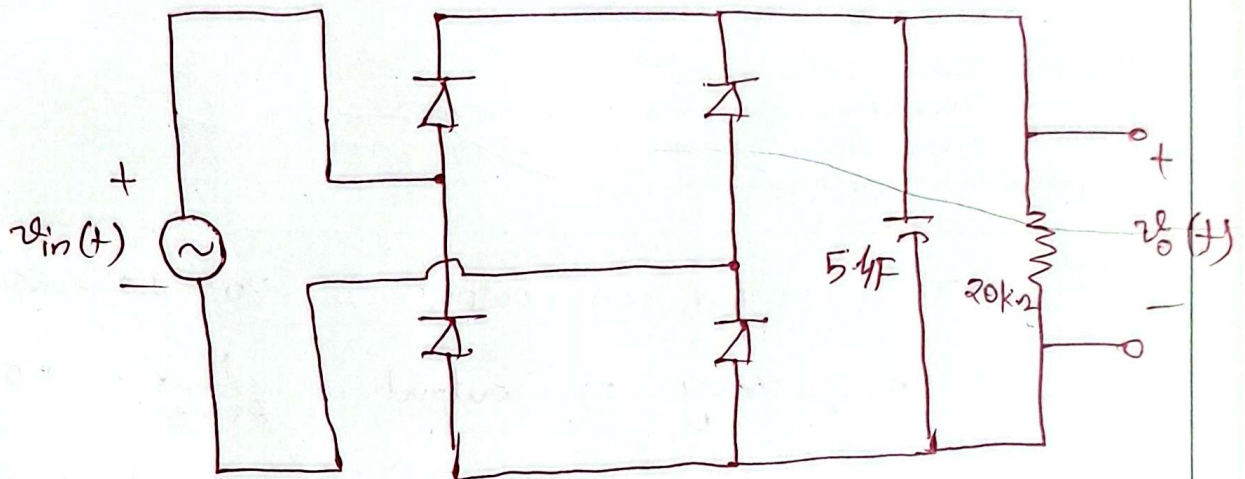

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Proper units must be included for all calculated values. Marks will be deducted for missing or incorrect units.
- ✓ Symbols have their usual meanings.

Question 1 of 3

[CO2] [4 marks]

For the rectifier circuit shown, the diodes D_1 , D_2 , D_3 , and D_4 have cut-in voltages of 0.5 V, 1.2 V, 0.5 V, and 0.8 V, respectively. The input voltage v_S is a sinusoidal waveform as plotted below. Sketch the output voltage v_O on the same grid as v_S .

(-) half cycles

D_2 & D_4
ON


Voltage drop =

$$1.2 + 0.8$$

$$= 2V$$

$$V_p = V_m - 2$$

$$= 2V$$

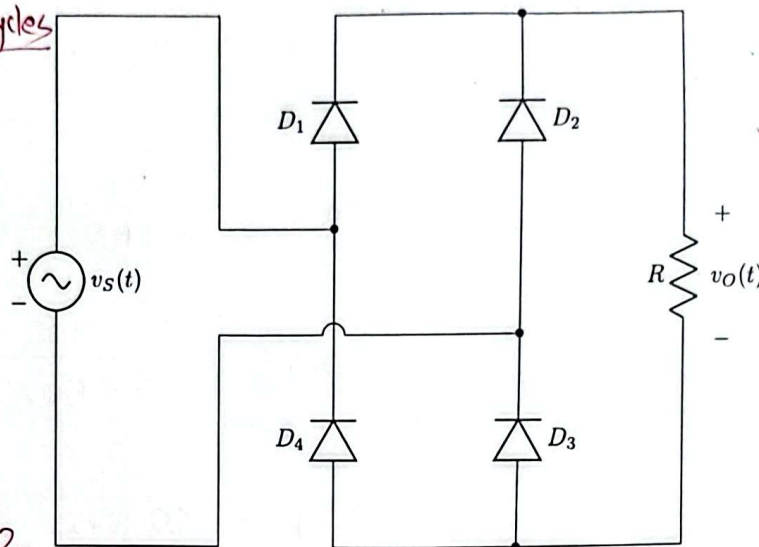

(+) half cycles

D_1 & D_3 ON


Voltage drop

$$= 0.5 + 0.5$$

$$= 1V$$

$$V_p = V_m - 1$$

$$= 3V$$

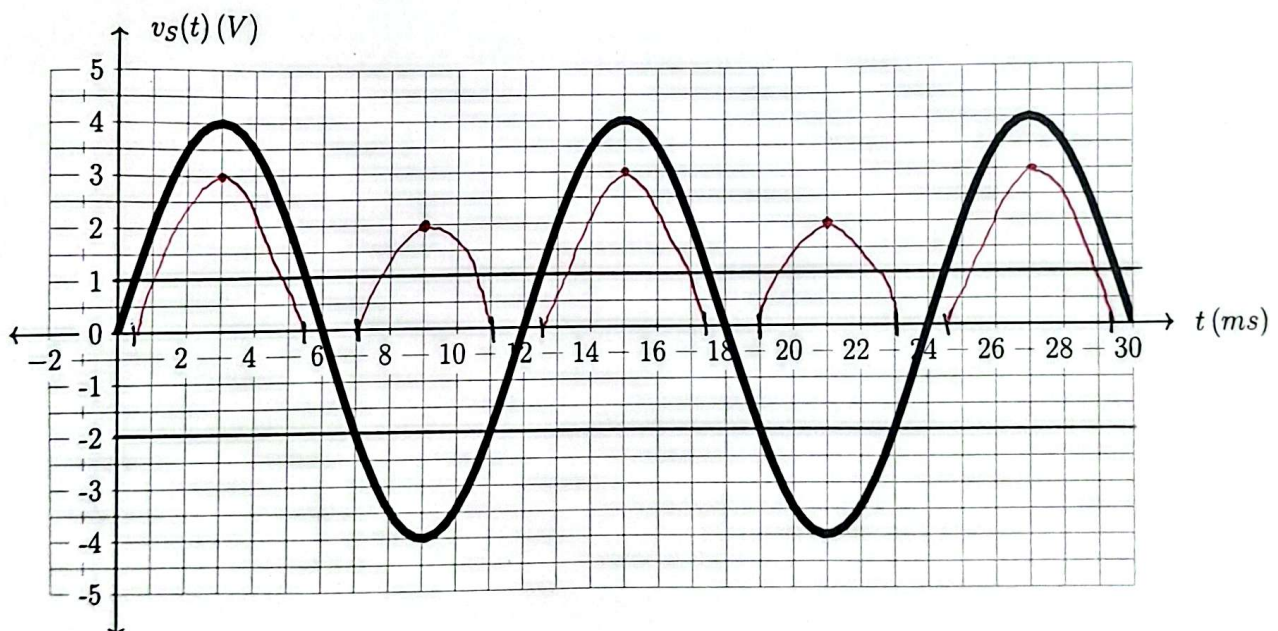

■ Question 2 of 3

[CO2] [6 marks]

A 6V amplitude, 50Hz sinusoidal AC voltage is rectified and filtered using a FW rectifier with 8μF filter capacitor. The diodes used in the rectifier are identical and have a cut-in voltage of 0.6V. If the average output voltage is measured to be 4.5V, determine the value of the load resistance.

$$V_m = 6V$$

$$f = 50\text{Hz}$$

$$C = 8 \times 10^{-6}\text{F}$$

$$V_{D0} = 0.6V$$

$$V_{avg} = V_{DC} = 4.5V$$

$$V_p = V_m - 2V_{D0} = 4.8V$$

$$V_{avg} = V_p - \frac{V_r}{2}$$

$$\Rightarrow V_r = 2(V_p - V_{avg})$$

$$= 2(4.8 - 4.5)$$

$$= 0.6V$$

$$V_r = \frac{V_p}{2fRC}$$


$$\Rightarrow 0.6 = \frac{4.8}{2 \times 50 \times R \times 8 \times 10^{-6}}$$

$$\Rightarrow R = 10\text{ k}\Omega$$

■ Question 3 of 3

[CO3] [10 marks]

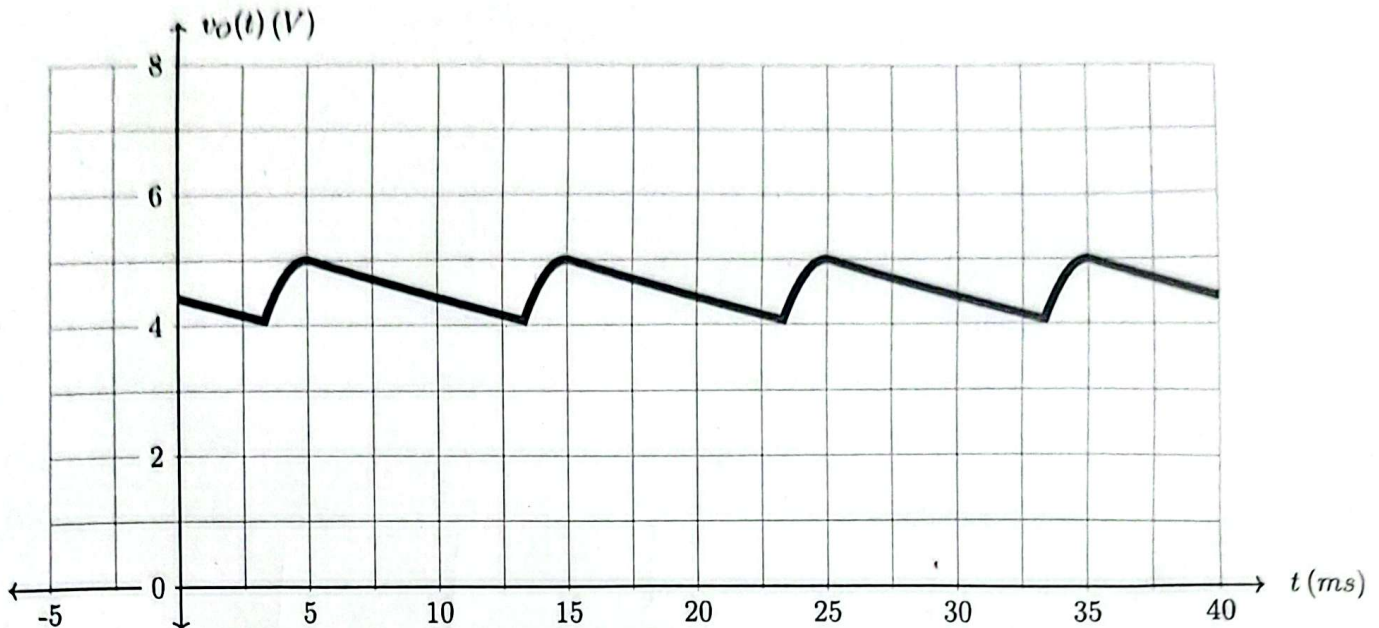The following is the rectified output of an AC sinusoidal voltage at 50 Hz frequency, applied to a load of 10 k Ω . The diode(s) used in the rectifier have a cut-in voltage of $V_{D0} = 0.6$ V.



- (a) [2 marks] What type of rectifier was used?
 (b) [4 marks] What is the filter capacitance value used in the rectifier design?
 (c) [2 marks] Write an expression for the input voltage as a function of time t .
 (d) [2 marks] Draw the circuit diagram of the rectifier.

(a) Time period of output = $15 - 5 = 10$ ms
 Frequency of output = $\frac{1}{10 \text{ ms}} = 100$ Hz
 As output frequency = $2 \times$ Input frequency
 It was **FW rectifier**

(b) From the plot,
 $V_p = 5$ V, $V_r = 1$ V

$$V_r = \frac{V_p}{2fRC}$$

$$\Rightarrow 1 = \frac{5}{2 \times 50 \times 10 \times 10^3 \times C}$$

$$\Rightarrow \boxed{C = 5.4 \text{ F}}$$

$$\left\{ \begin{array}{l} f = 50 \text{ Hz} \\ R = 10 \text{ k}\Omega \\ V_{D0} = 0.6 \text{ V} \end{array} \right.$$

(c) $v_{in}(t) = V_m \sin(2\pi f t)$

$$V_m = V_p + 2V_{D0} = 5 + 2 \times 0.6 \\ = 6.2V$$

$$v_{in}(t) = 6.2 \sin(2\pi 50t) (V)$$

(d)

